

Nyquist Rate DACs


Nan Sun
Tsinghua University
nansun@Tsinghua.edu.cn

Overview


- Topologies
 - Resistor string DAC
 - Voltage switching DAC
 - Current steering DAC
 - Switched capacitor DAC
 - R-2R DAC
- Current steering DAC architectures
- Static errors
- Dynamic errors
- Example implementations

Resistor-String Voltage DAC

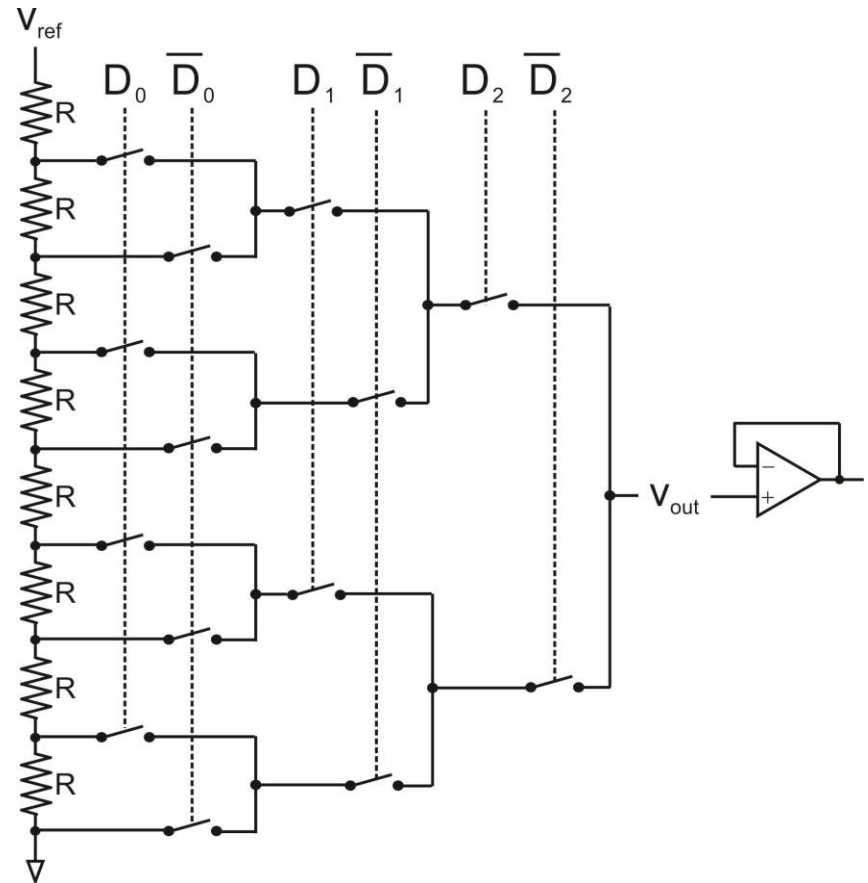- Digitally controlled potentiometer
- Advantages
 - Simple ☺
 - Monotonic ☺
- Unsuitable for high-speed ☹
 - Tree-type of decoder has a large resistance
 - Large and unequal RC time constant at the output
 - Add an opamp will help
 - High power & low-speed
- Unsuitable for high-resolution ☹
 - Too many resistors & switches




Voltage Switching DAC

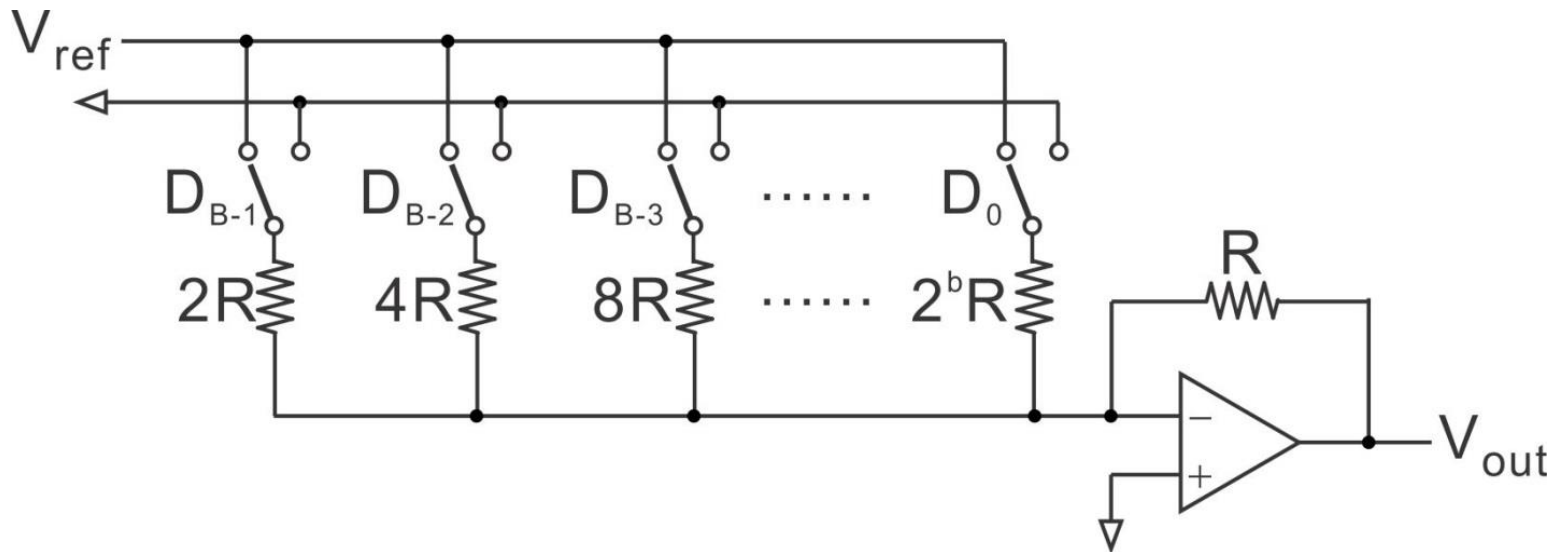

- Use analog adders
- Nonlinearity due to nonzero switch turn-on resistance

Current Steering DAC

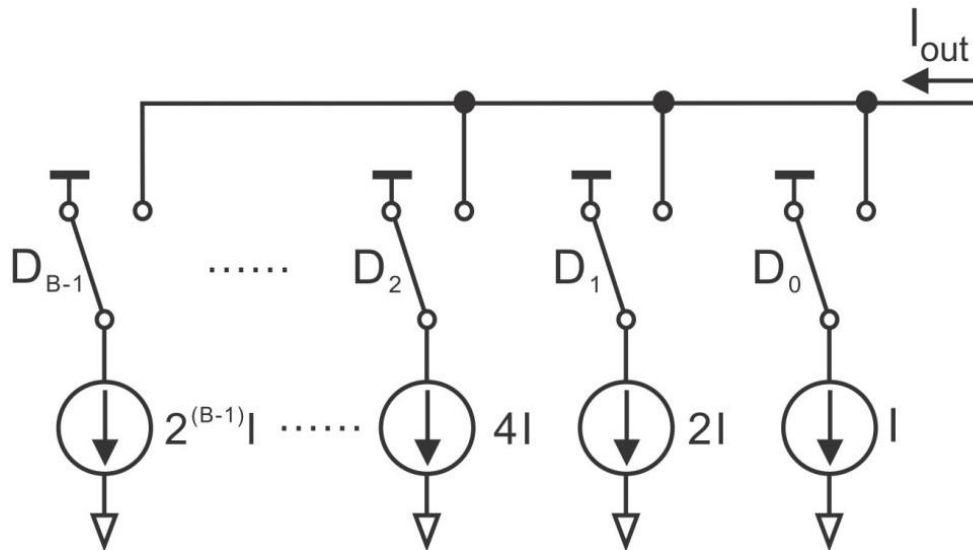


For voltage output

Scheme 1




Scheme 2

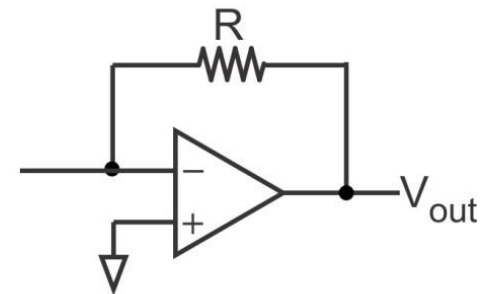


- MOS switches are much better at switching current than voltage!
- Can build very good current sources with high impedances
- Suitable for high speed 😊
 - Avoid the use of opamps
 - Small RC time constants at the output


Switched Capacitor DAC

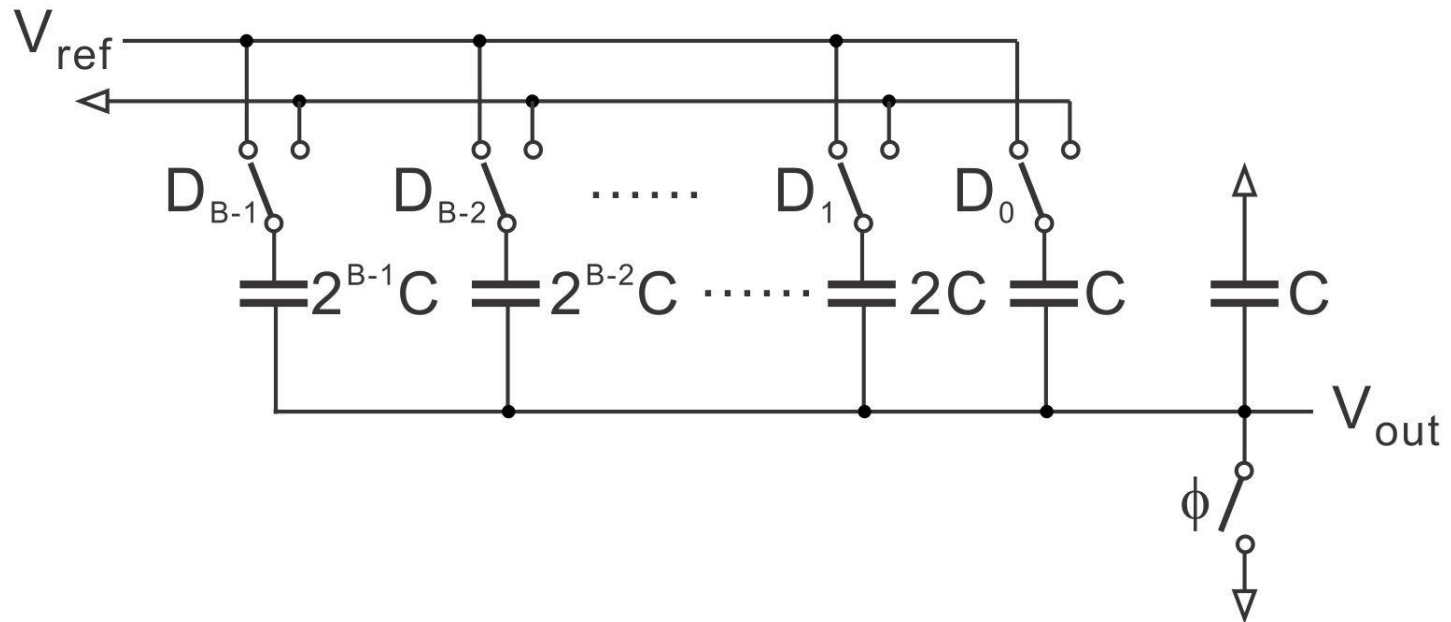

Initialization Phase ($\phi = V_{dd}$)

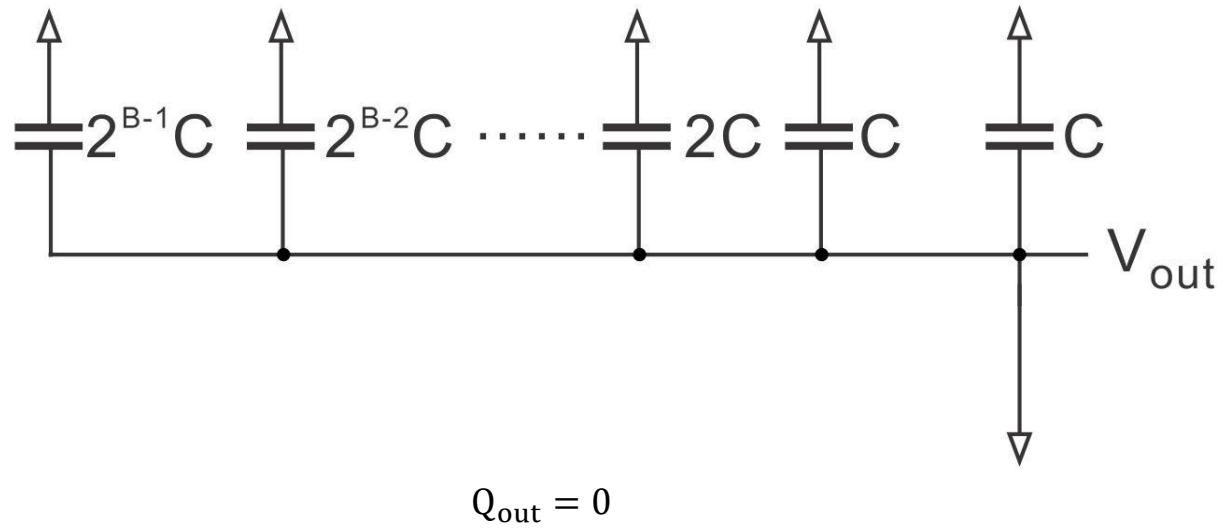

Evaluation Phase ($\phi=0$)

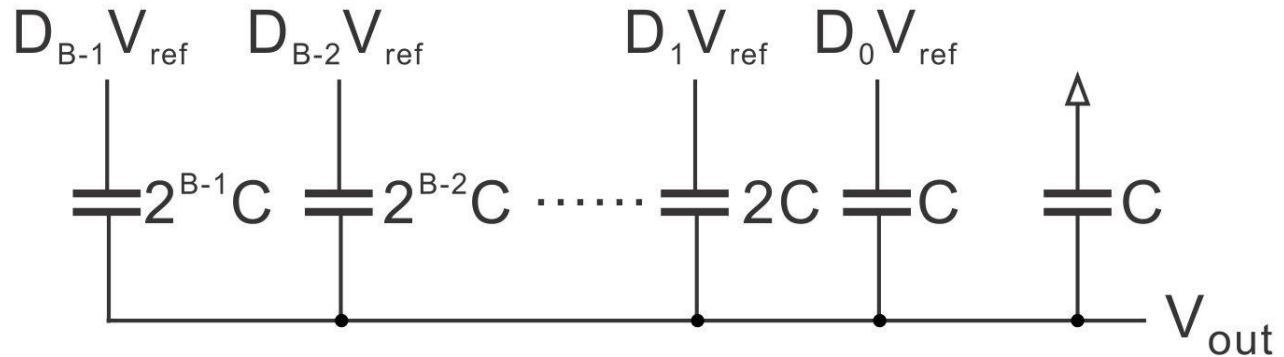


- Due to charge conservation:

$$Q_{out} = CV_{out} + \sum_{i=0}^{B-1} (V_{out} - D_i V_{ref}) 2^i C = 0$$


$$V_{out} = V_{ref} \sum_{i=0}^{B-1} 2^{i-B} D_i$$

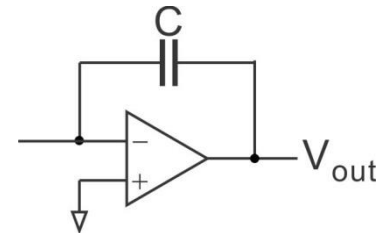- Nonlinear cap at V_{out} is a big problem
 - Use an opamp with a feedback cap




R-2R DAC Concept (voltage mode)

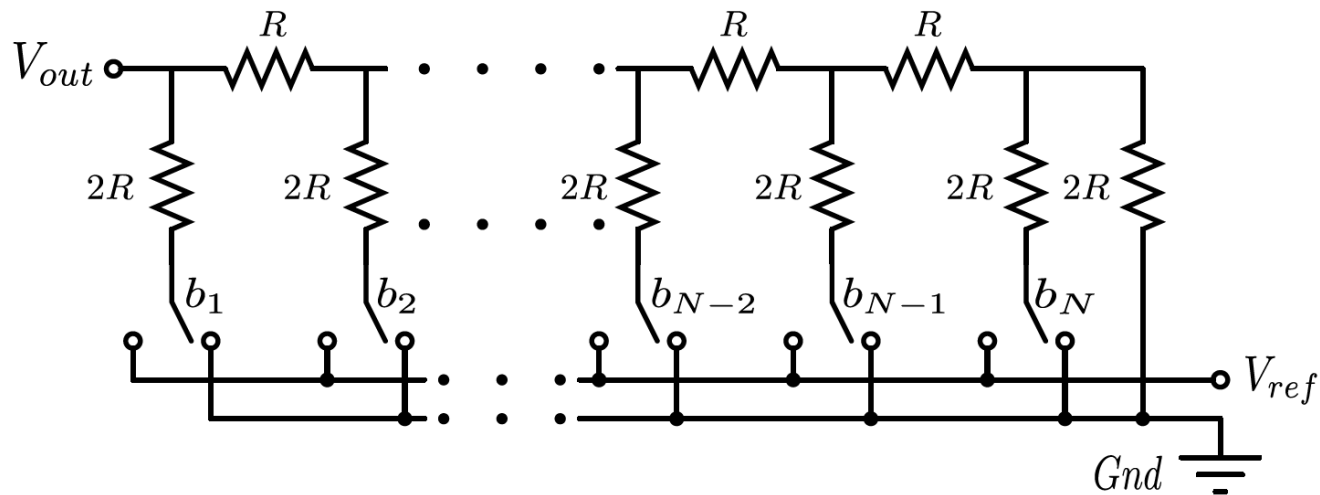- Aforementioned techniques all require large device ratios
 - Assuming the size of the smallest device is fixed by matching requirement, a large device ratio leads to a large area
- Is it possible to get exponentially weighted voltage/currents by using similar sized devices?
 - R-2R ladder




R-2R DAC Concept (current mode)

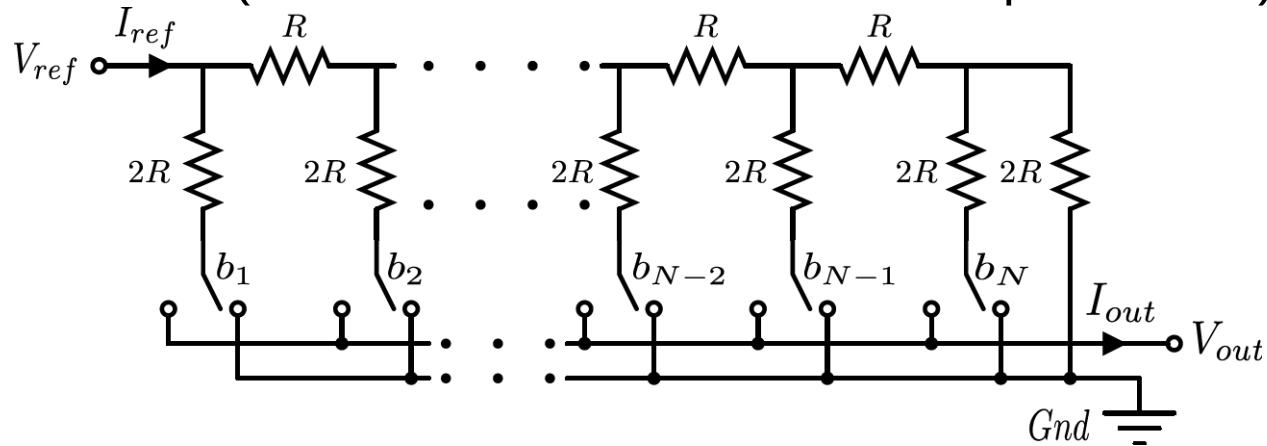- Current mode (need a FB-OTA to buffer the output current)




- Output impedance is code dependent

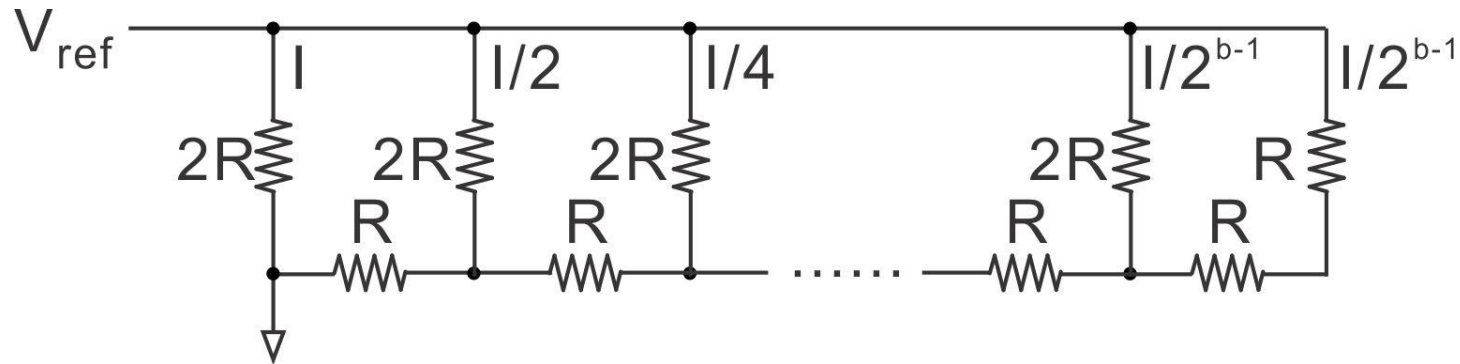


- How to pull the current out?

R-2R DAC Implementation

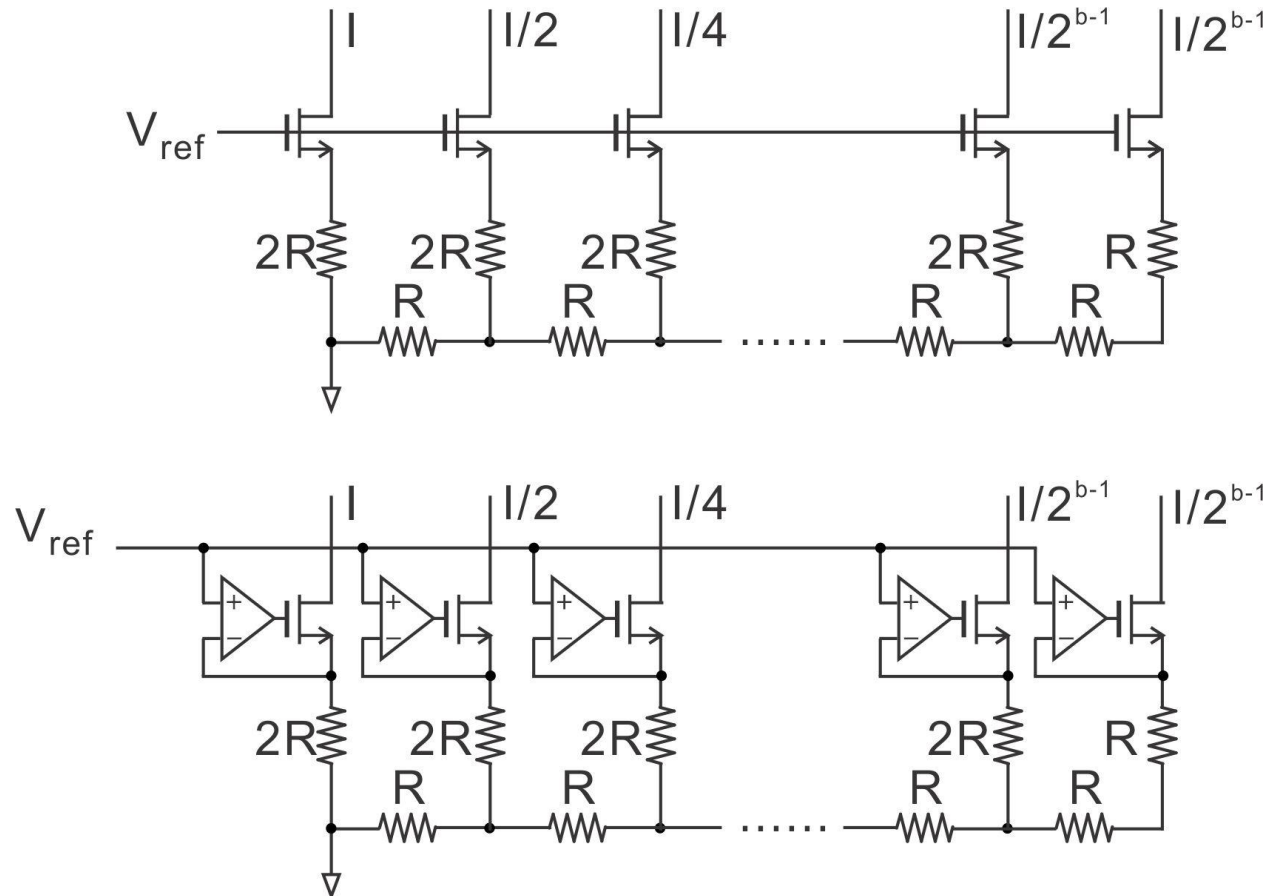

- OTAs can be used to remove V_{GS} variations
 - Extra power, area, and slow

Drain R-2R Ladder

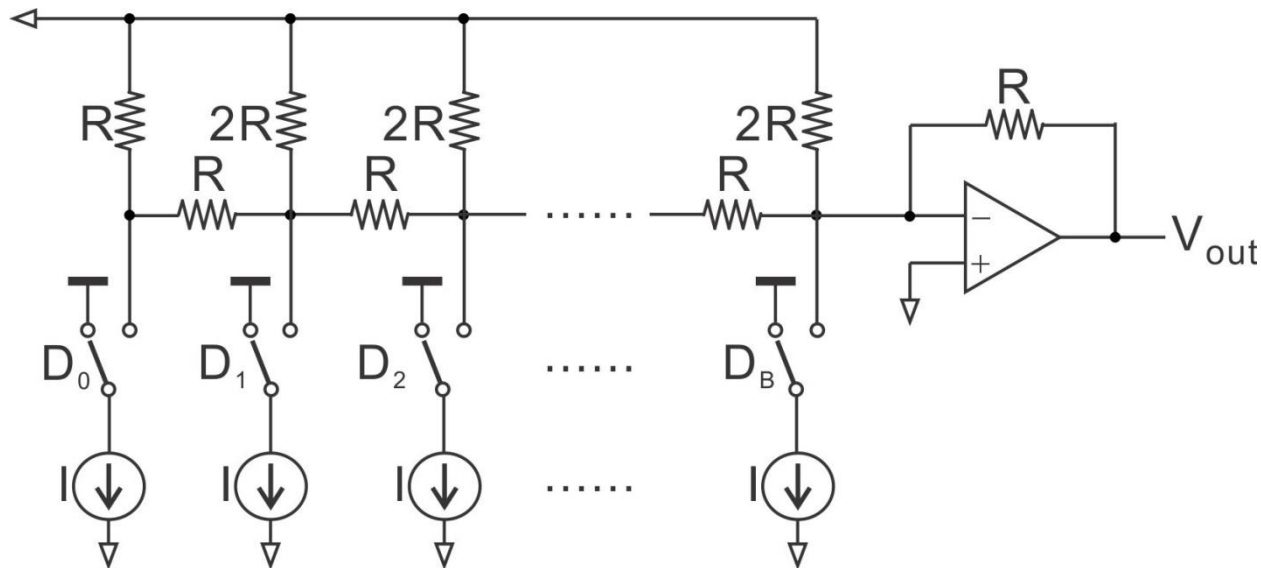


- This topology ensures the same current
- Low output impedance of R-2R ladder → necessitate opamp → unsuitable for high speed
- Nowadays, most high-speed DACs are current-steering DACs
 - We will focus on current-steering DACs from now on

Overview


- Topologies
- Current steering DAC architectures
 - Binary weighted DAC
 - Thermometer DAC
 - Segmented DAC
- Static errors
- Dynamic errors
- Example implementations

Binary Weighted Current Steering DAC

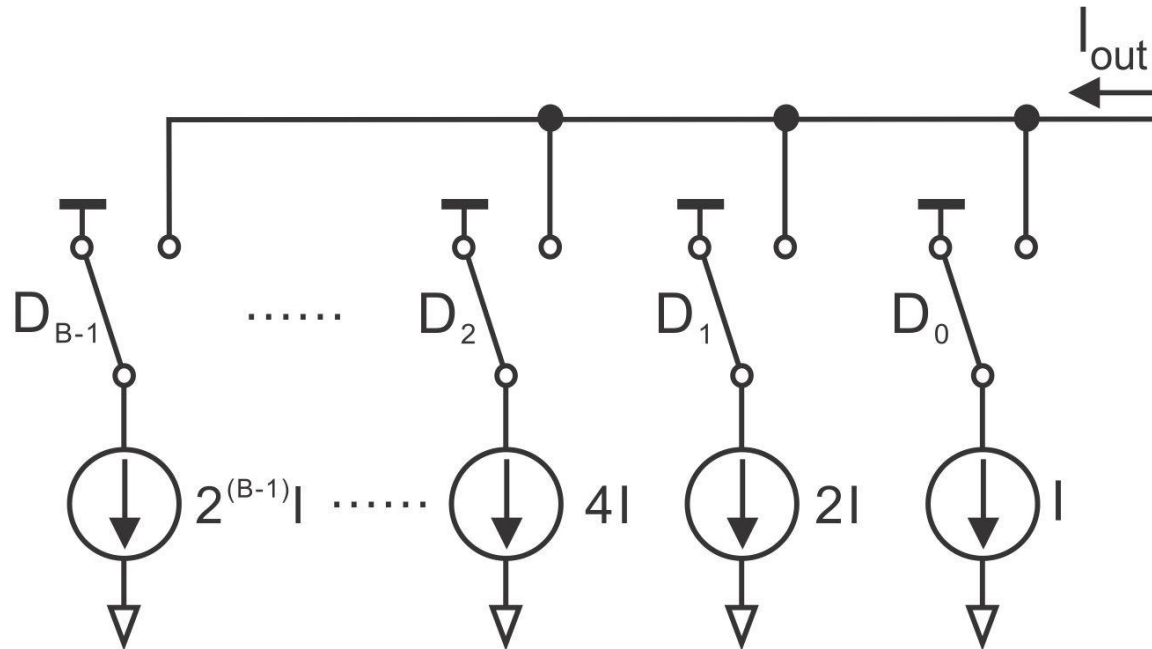


- Simple structure 😊
- No encoder needed 😊
- How to match the current sources?

How to Achieve Good Matching

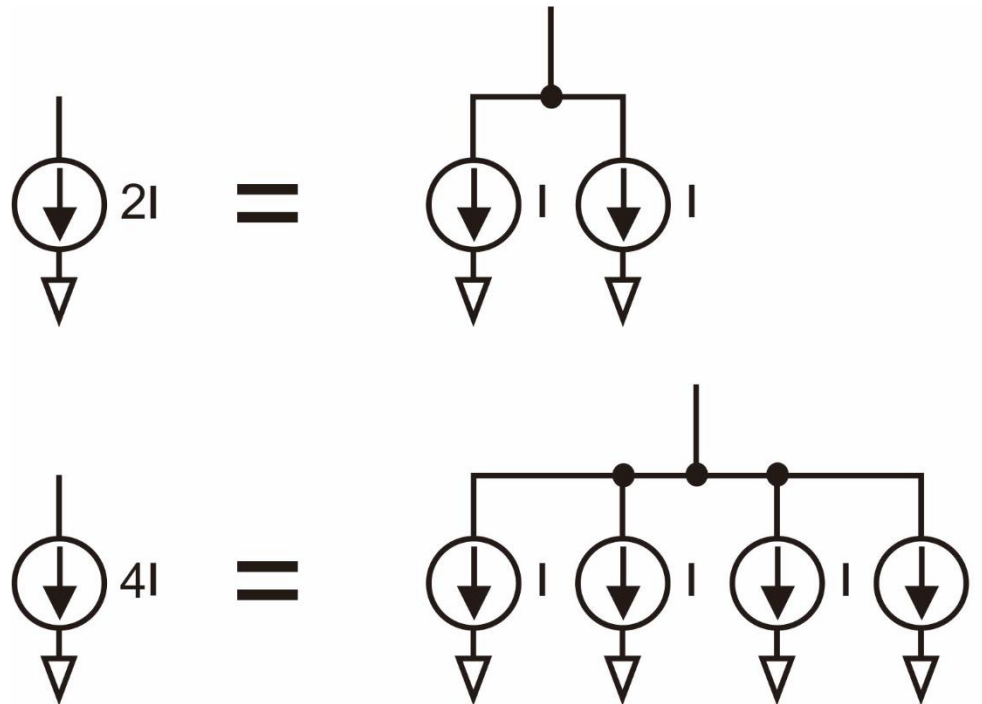


- All current sources are made by identical unit current sources put in parallel.

Binary Weighted DAC Principle

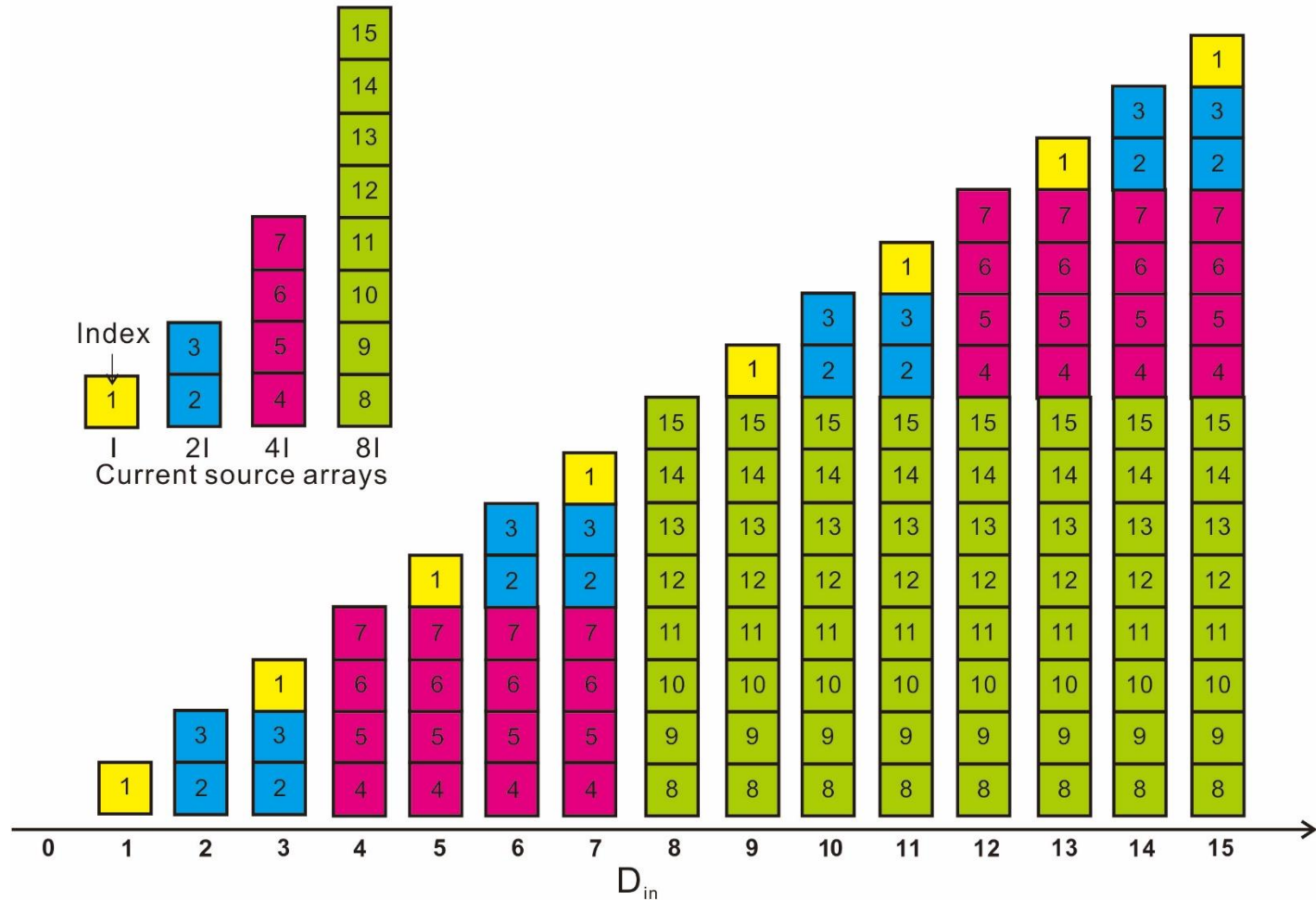


MSB Transition Problem

Cannot ensure monotonicity ☹

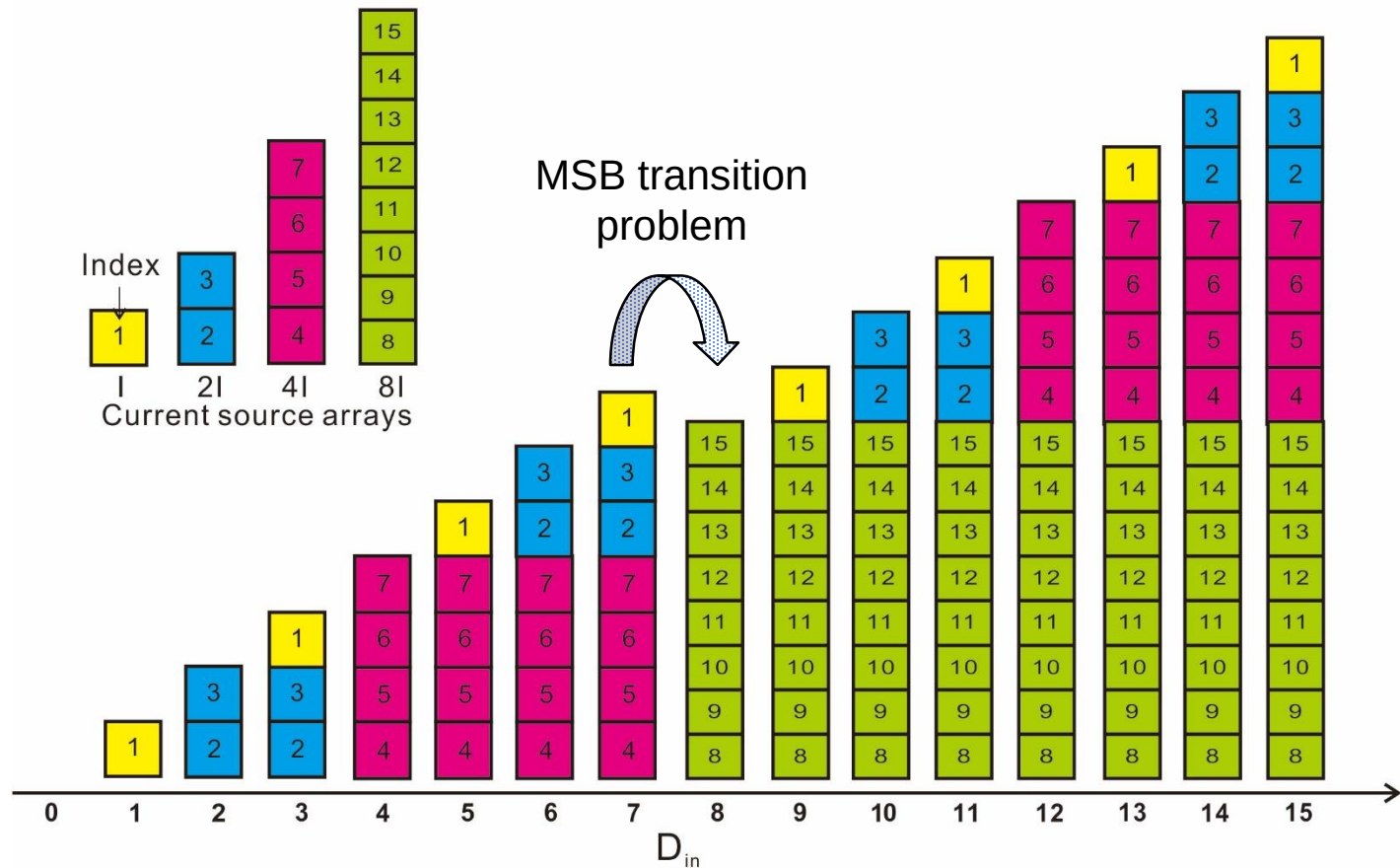


Thermometer Current Steering DAC

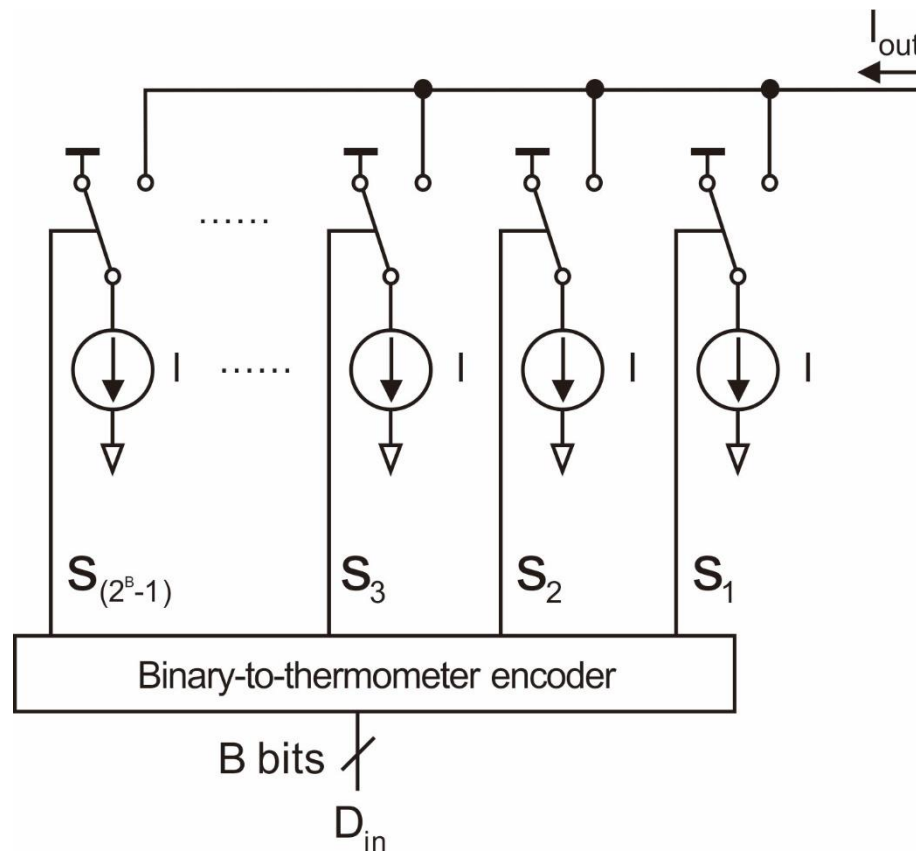


- Inherently monotonic 😊
- Need large encoder with $2^B - 1$ outputs ☹
 - Impractical for large B


Thermometer DAC Principle

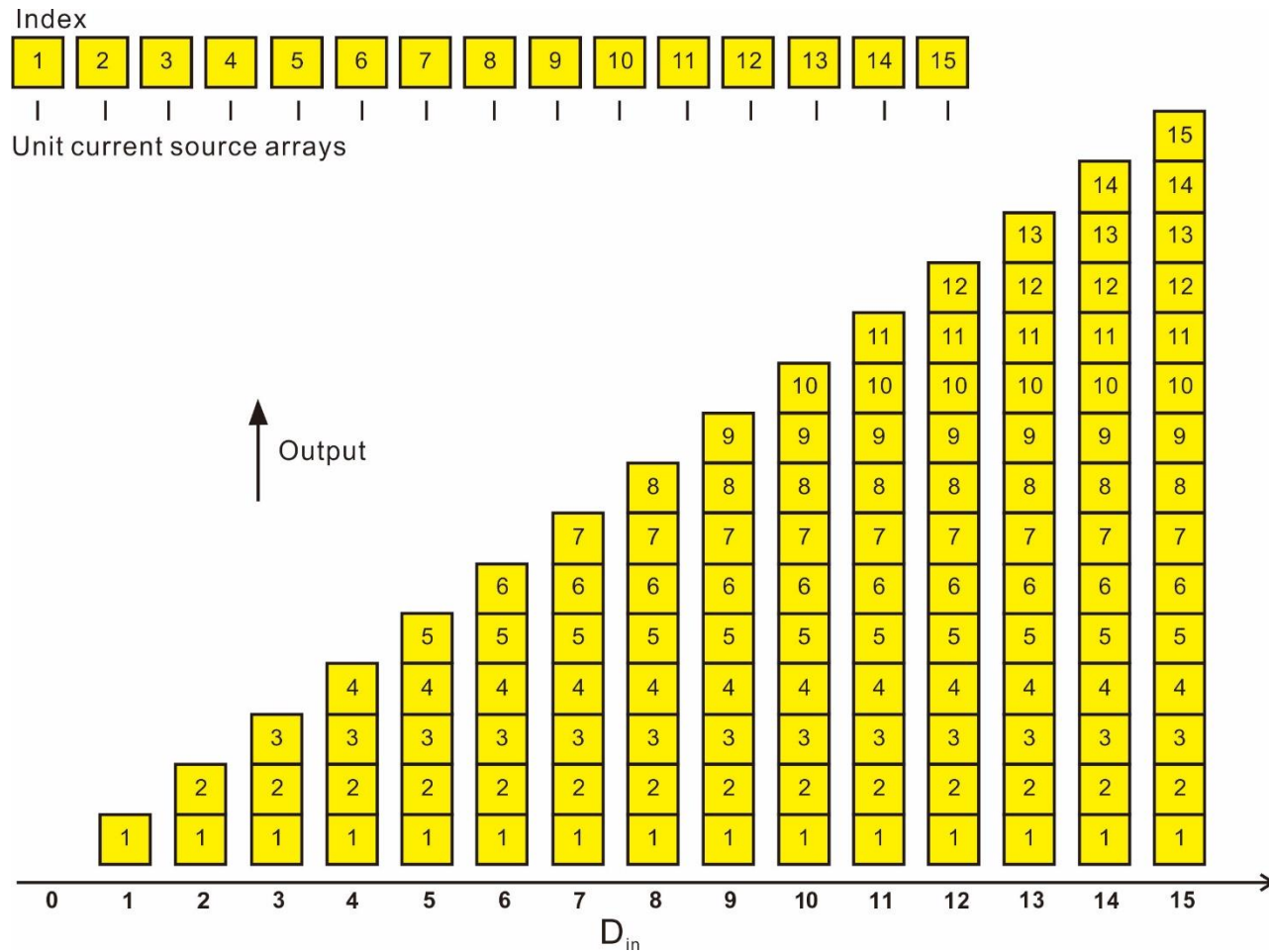

Monotonicity Guaranteed

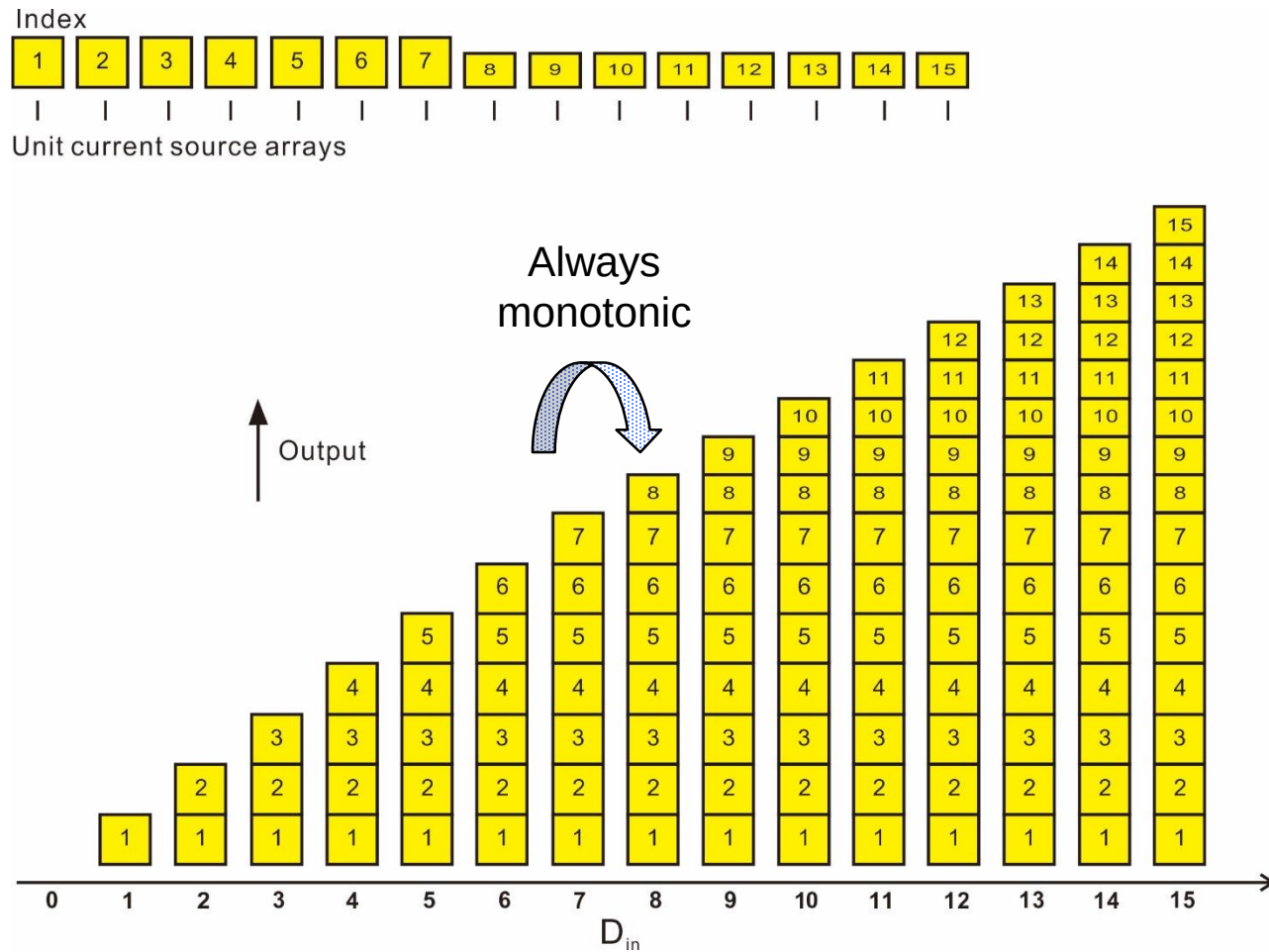


Segmented DAC

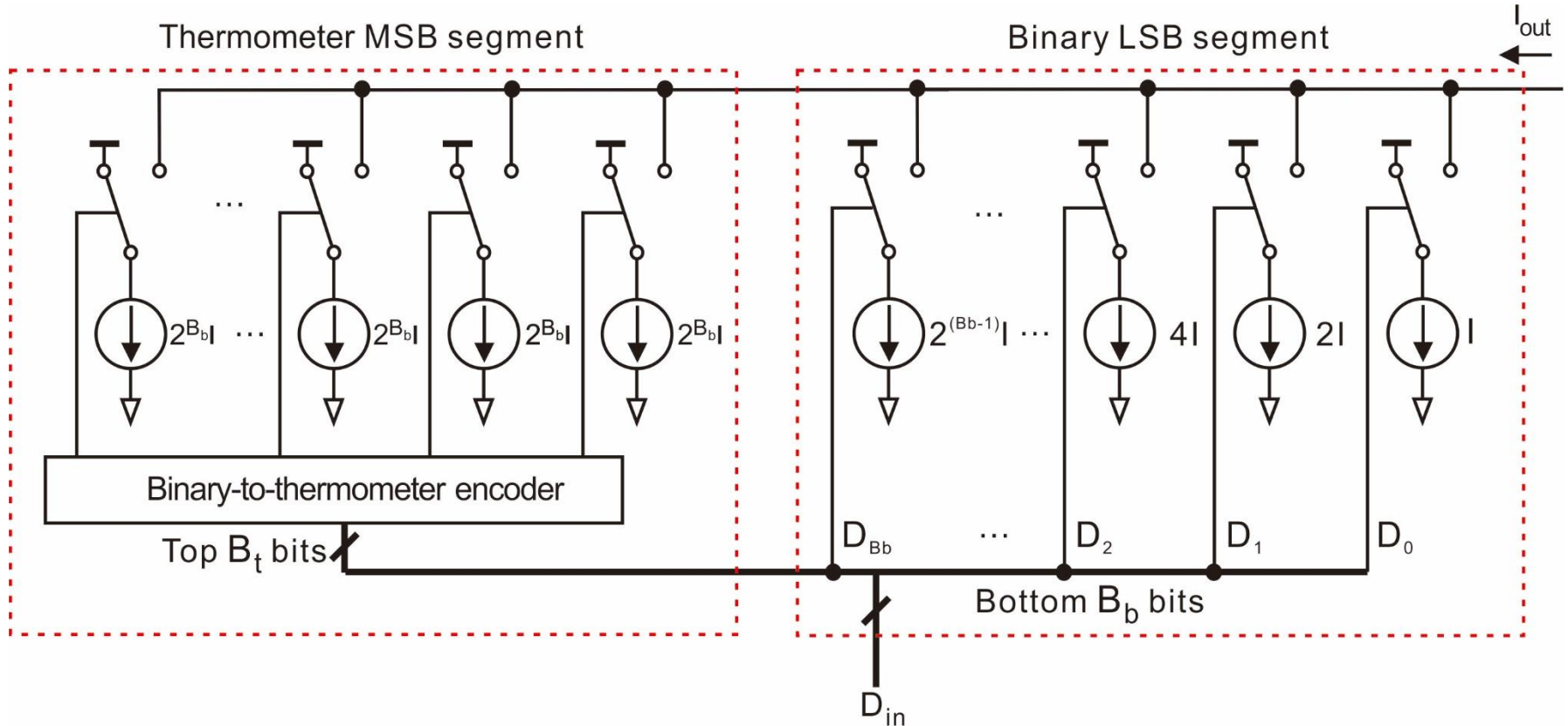


- Binary segment with B_b bits; thermometer segment with $B_t = B - B_b$ bits
- Easier to ensure monotonicity than purely binary DAC 😊
- Smaller encoder than purely thermometer DAC 😊

Segmented DAC (2-2)

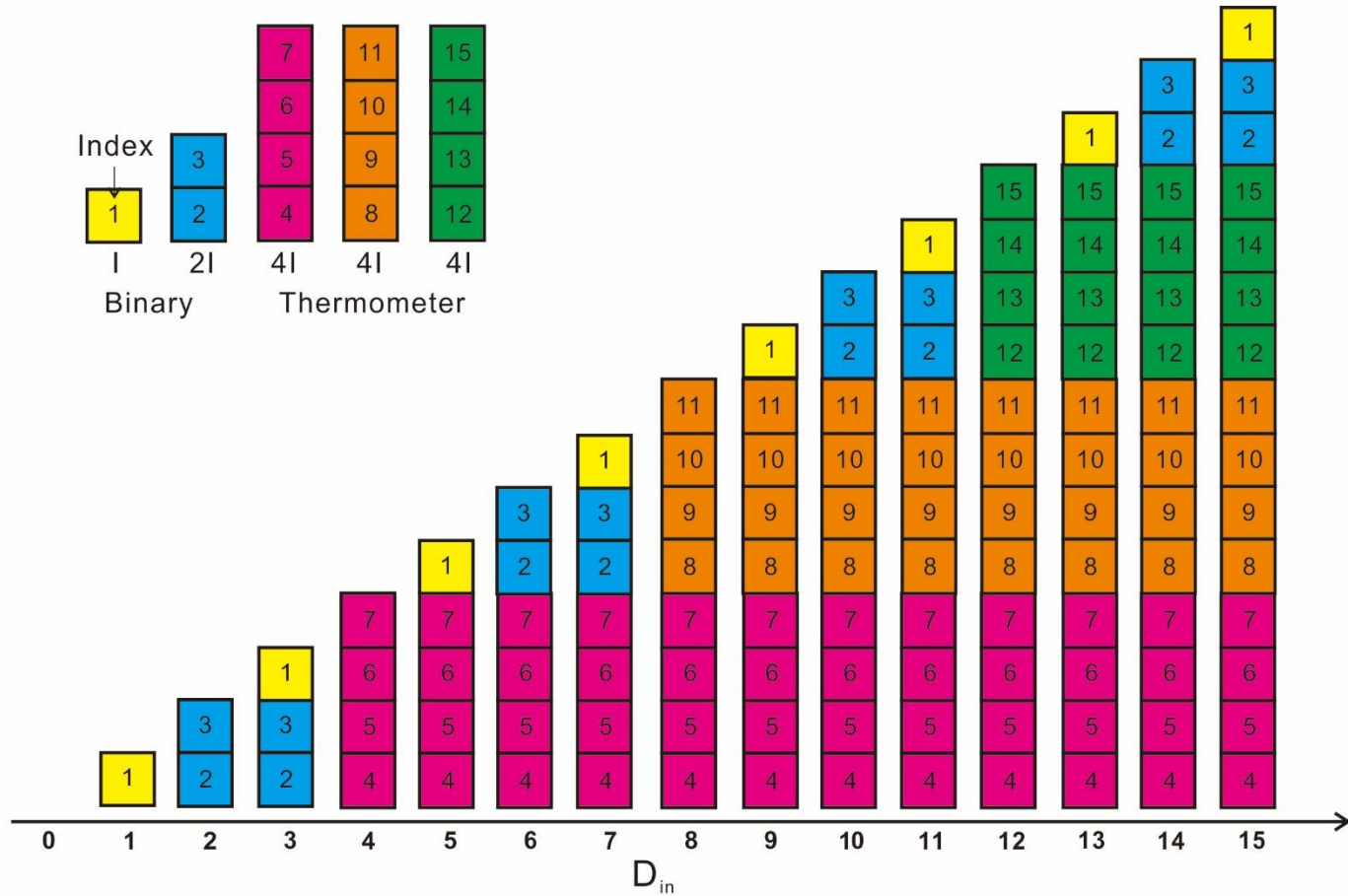

Easier to Ensure Monotonicity

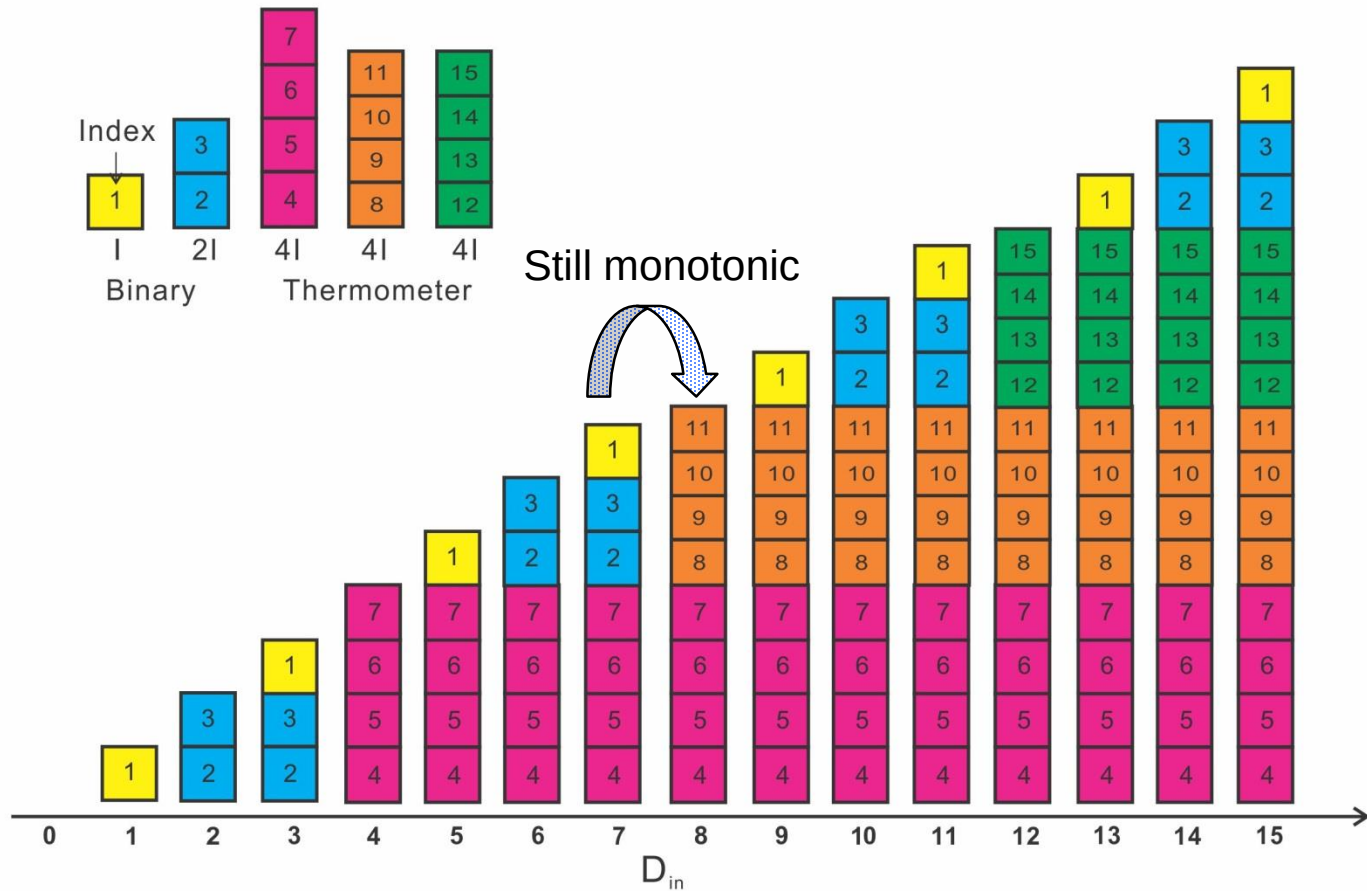

Overview


- Topologies
- Current steering DAC architectures
- Static errors
 - Mismatch
 - Finite output impedance
- Dynamic errors
- Example implementations

Systematic Mismatch


- DNL and INL due to unit element mismatch
- Systematic mismatches
 - IR drop due to contact and wiring resistance
 - Process artifact
 - Gradient
 - Well proximity effect
 - Length of diffusion (shallow trench isolation)
 - Metal coverage
- Systematic mismatches can be mitigated through proper layout
 - Add dummy cell
 - Common centroid layout

Layout Techniques to Reduce Gradient Errors


Dummy cell

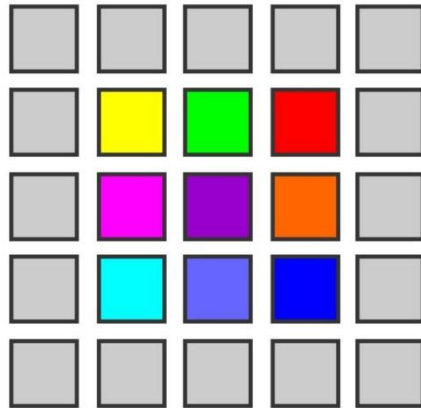

Common centroid layout

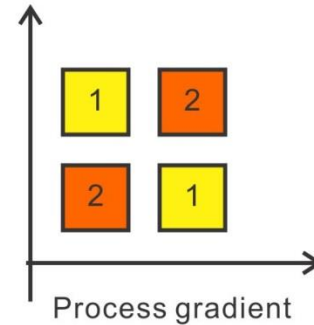



More complicated

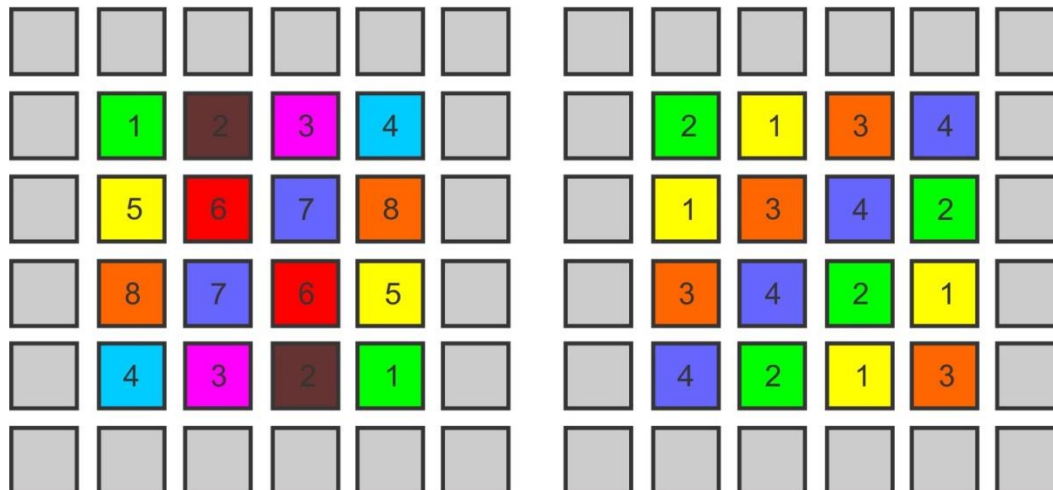

Gradient Errors

- In modern CMOS process, parametric gradients are generally well below 1 %/cm (1ppm/ μm). They are smaller than other nonidealities.
 - Most mixed-signal blocks are spread out over less than 2mm
 - Most IP-blocks are smaller than $100 \times 100 \mu\text{m}^2$
- Use common centroid layouts only for very big components


Well Proximity Effect

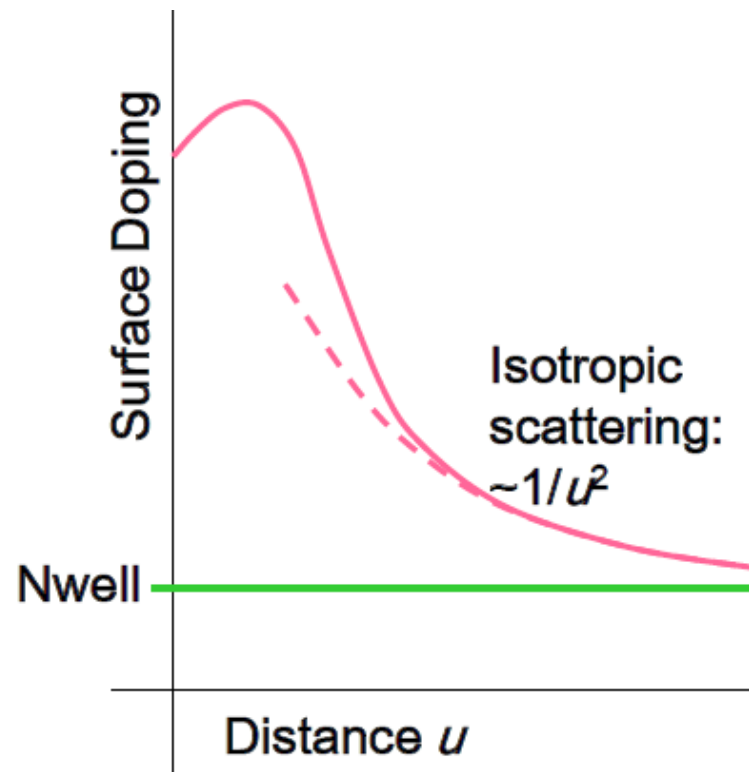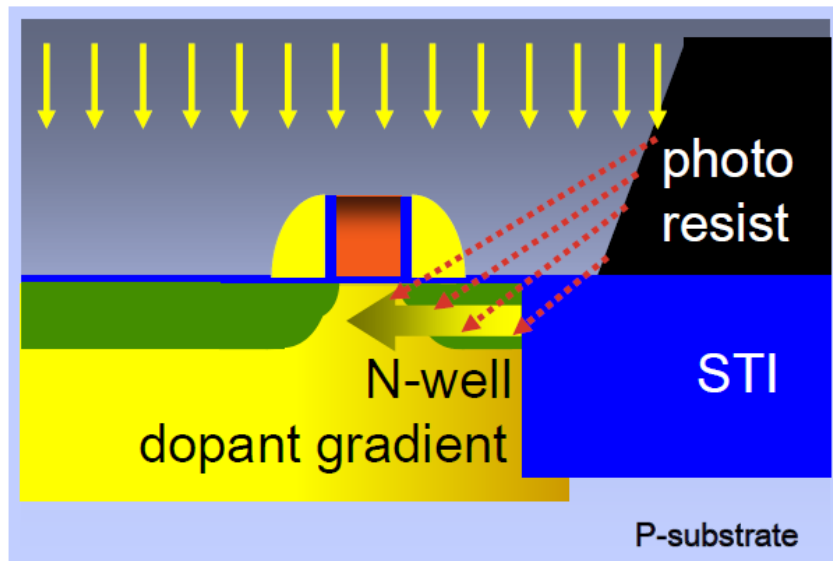

From H. Tuinhout, CICC 13', Education Session 2.


see: T.B. Hook et al.,
IEEE Trans. on Electron Devices,
Vol. 50, No. 9, pp. 1946-1951, 2003.

WPE Effect Study (1)

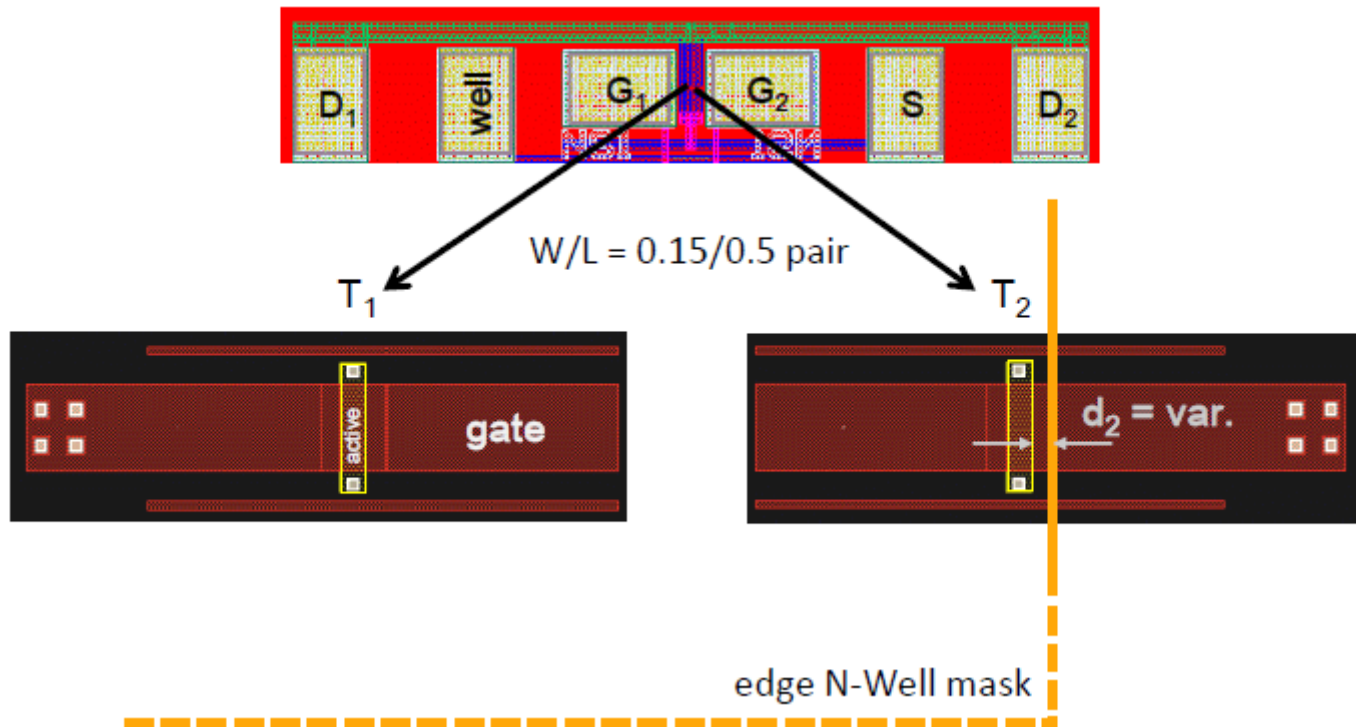

From H. Tuinhout, CICC 13', Education Session 2.

WPE Effect Study (2)

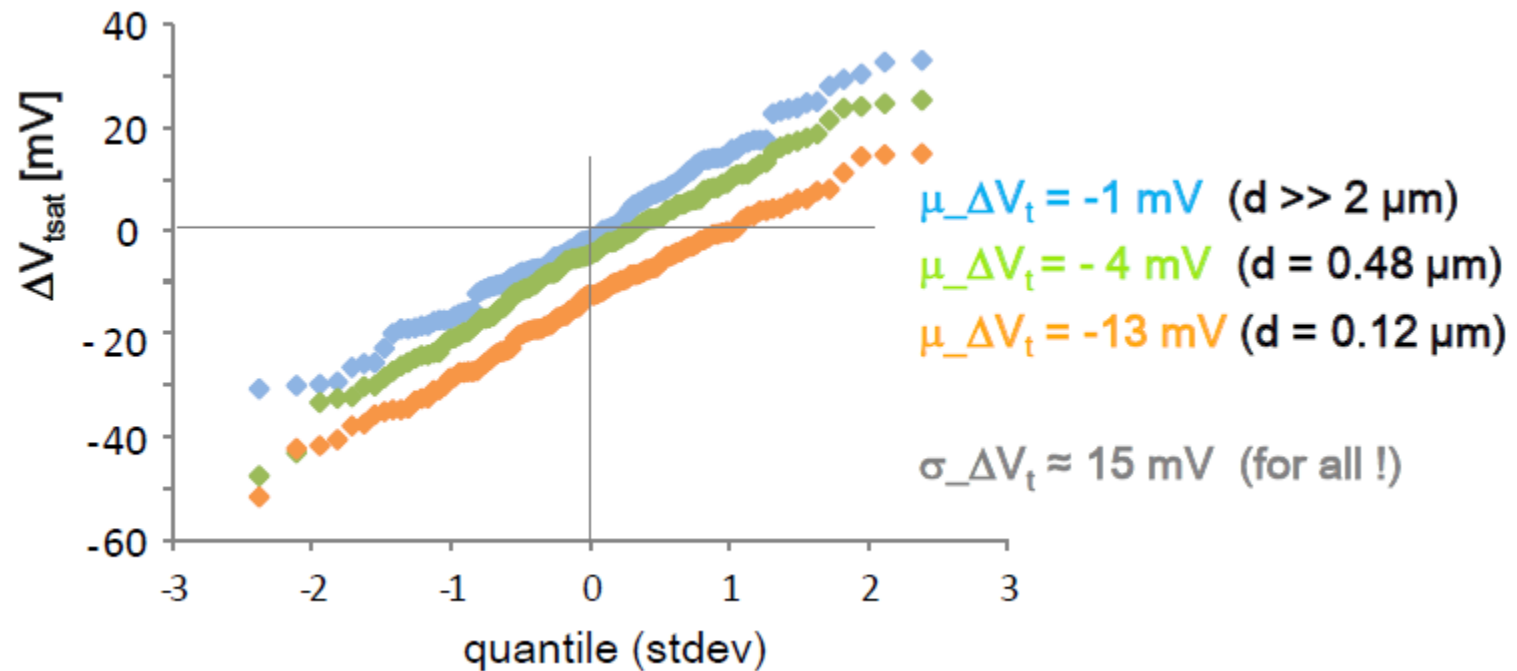


From H. Tuinhout, CICC 13', Education Session 2.

Well Proximity Effect (WPE)

- WPE depends on:
 - Distance of well edge to active region
 - Well implant dose density and energy
 - Oxide thickness and channel doping profile of the devices
- WPE impacts:
 - V_T variation (up to 30mV per well edge)
- Method to alleviate WPE problem
 - Ensure well-to-active-region distance $>1\mu\text{m}$




Shallow Trench Isolation (STI)

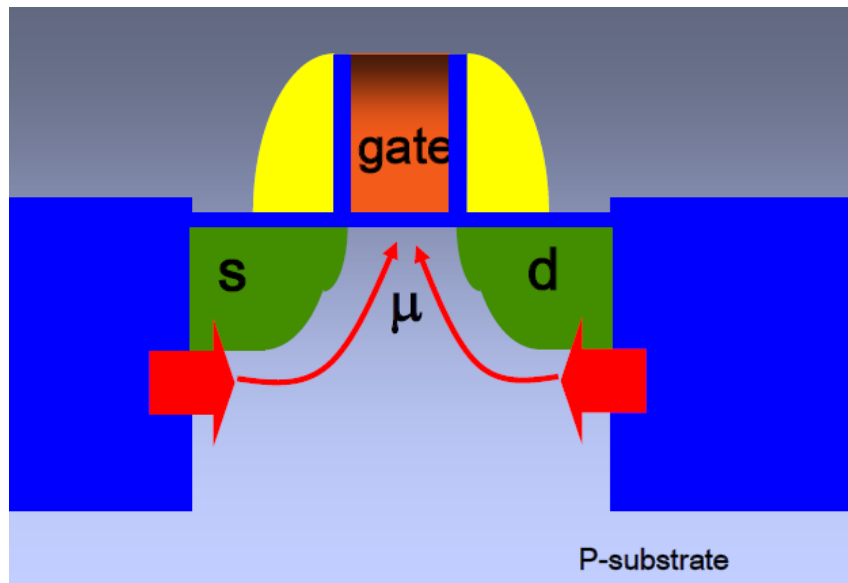

- STI produces compressive mechanical stress
 - Increases hole μ , reduces electron μ
 - Stress effect proportional to inverse of distance (length of diffusion)
 - Makes device current dependent on layout environment

From H. Tuinhout, CICC 13', Education Session 2.


STI Effect Study (1)

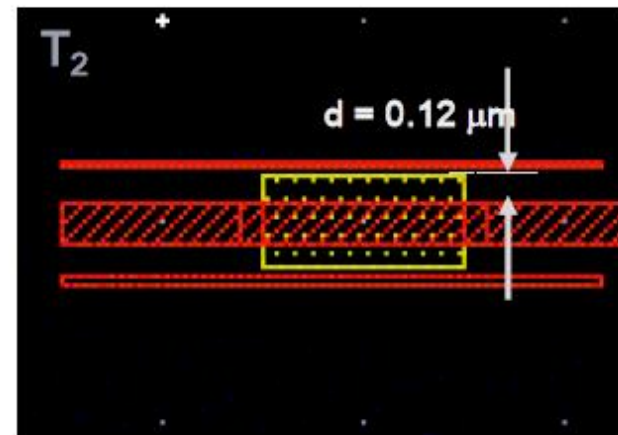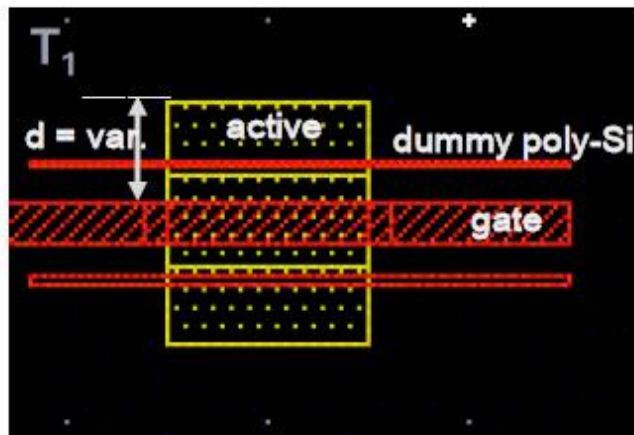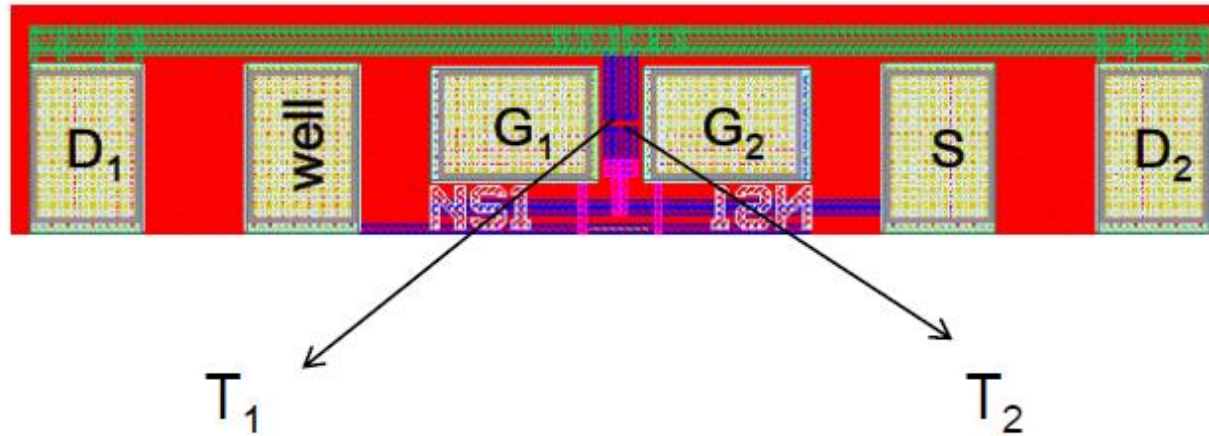

From H. Tuinhout, CICC 13', Education Session 2.

STI Effect Study (2)

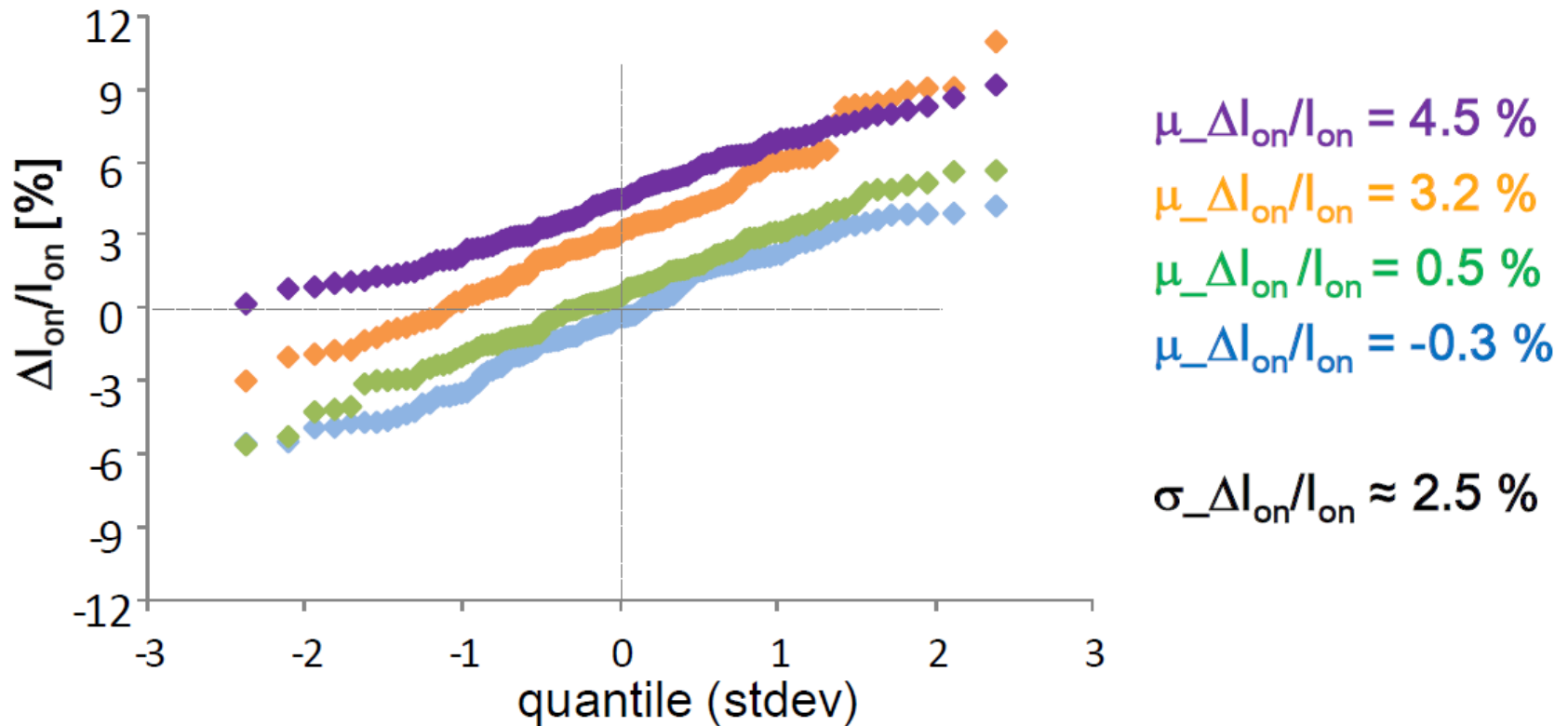
$d = 0.12$ (= reference), 0.14, 0.27 and 0.5 μm



From H. Tuinhout, CICC 13', Education Session 2.

Metal Induced Stress (1)

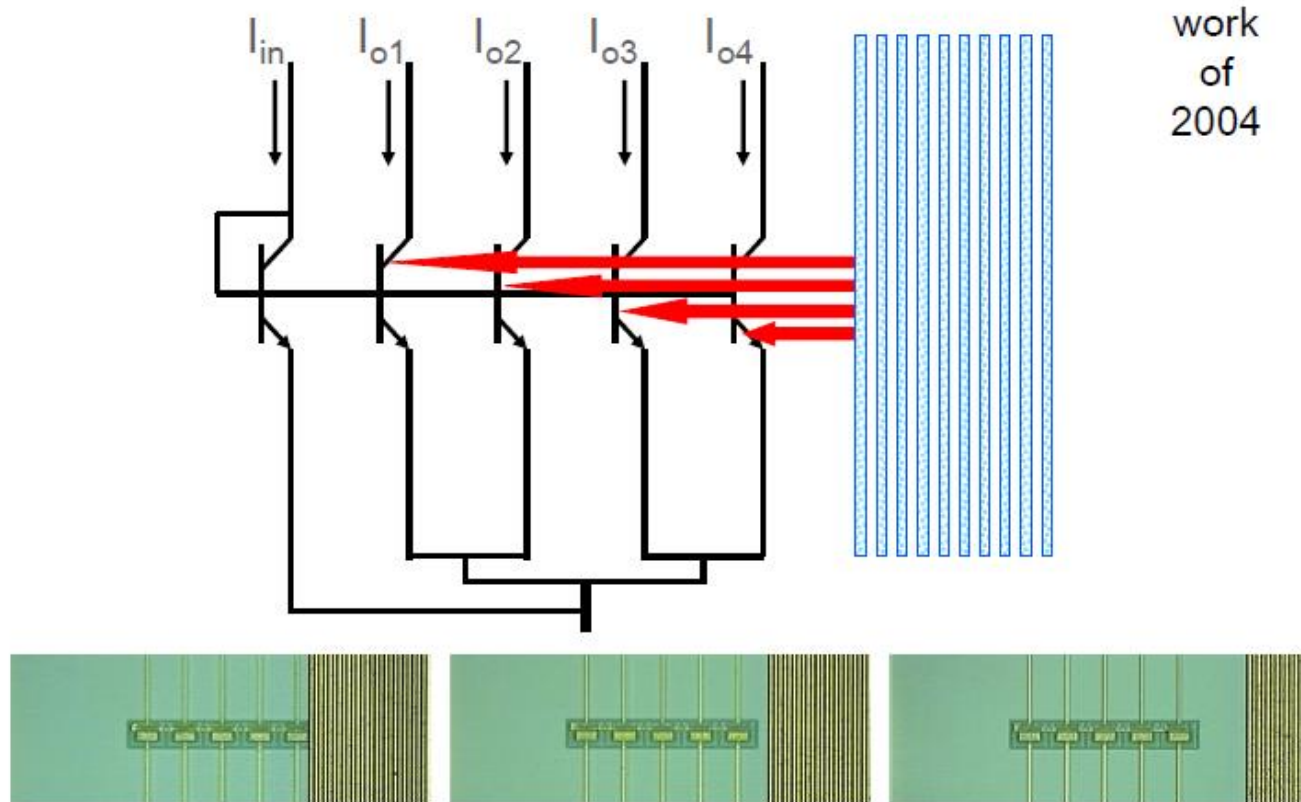
a useful set of experiment with current mirrors and distant stress sources



distance between T_4 and asymmetry is varied from minimum to 36 microns


From H. Tuinhout, CICC 13', Education Session 2.

Metal Induced Stress (2)

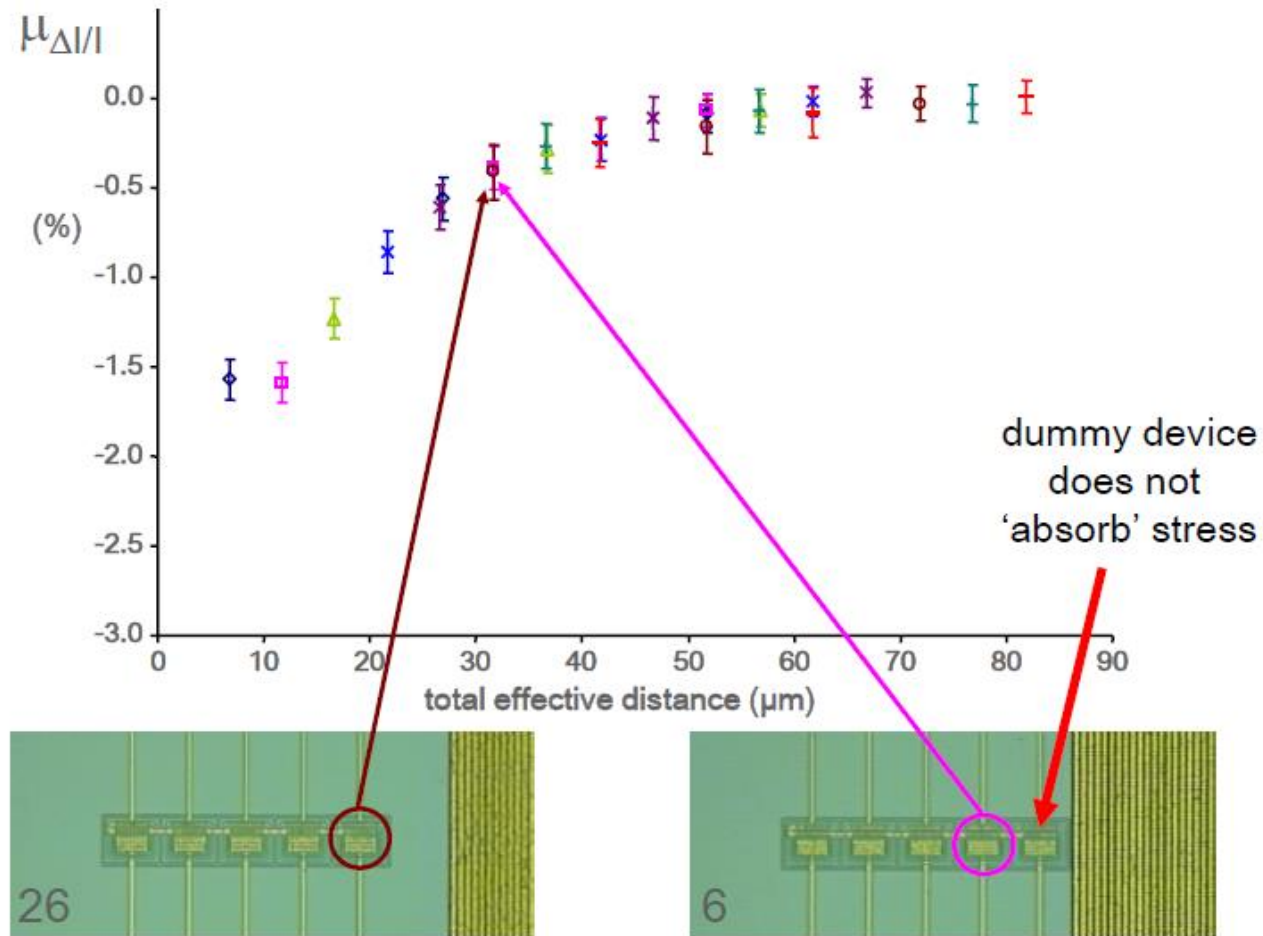

From H. Tuinhout, CICC 13', Education Session 2.

Metal Induced Stress (3)

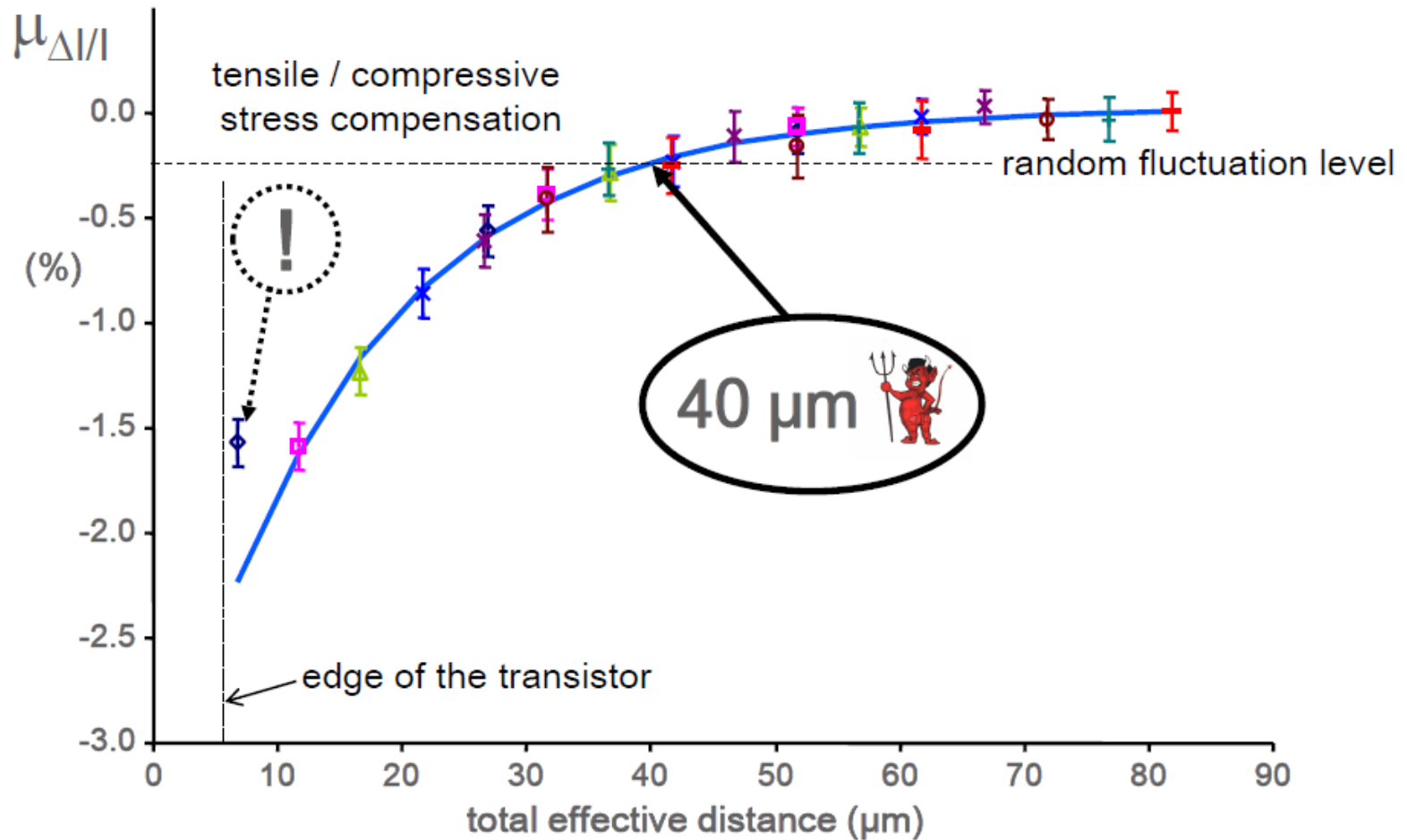

From H. Tuinhout, CICC 13', Education Session 2.

Random Mismatch

- Random mismatches are more fundamental and cannot be improved through layout
 - Random number of dopants (V_t variation)
 - Random etching (W & L variation)
- For a well-designed DAC, its nonlinearity should be limited by random mismatch, not systematic mismatch
- What is the distribution of the random mismatch:
 - Normal distribution (central limit theorem)
 - For a unit current source $I[k]$
 - Mean: I
 - Standard deviation: σ
 - We can write $I[k] = I(1 + \Delta I/I)$, then the percentage mismatch $\Delta I/I$ has:
 - Mean: 0
 - Standard deviation: $\sigma_{\Delta I/I}$


Mismatch in MOS Current Sources

$$\frac{\Delta I}{I} \approx \frac{g_m \Delta V_t}{I} + \frac{\Delta \beta}{\beta}$$

$$\Rightarrow \sigma_{\Delta I/I} = \sqrt{\left(\frac{g_m}{I}\right)^2 \sigma_{\Delta V_t}^2 + \sigma_{\Delta \beta/\beta}^2}$$

$$\sigma_{\Delta V_t} = \frac{A_{V_t}}{\sqrt{WL}}$$
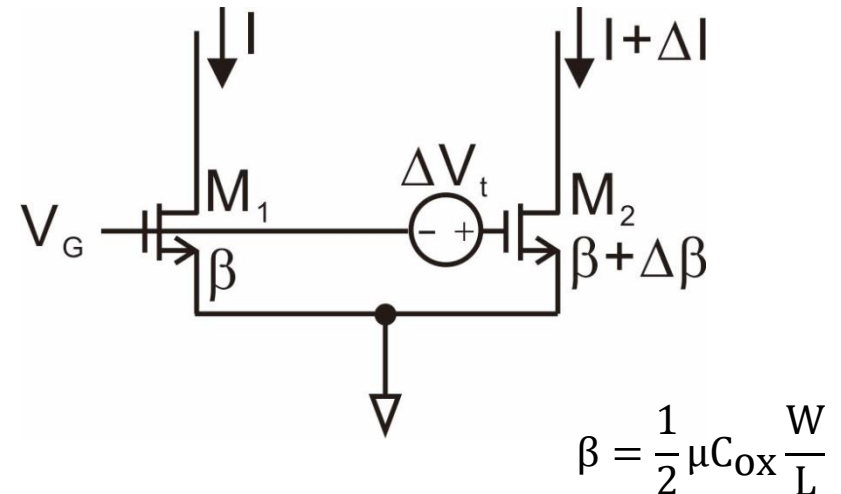
$$\sigma_{\Delta \beta/\beta} = \frac{A_\beta}{\sqrt{WL}}$$



- Example

- $W=10\mu\text{m}$, $L=0.1\mu\text{m}$, $g_m/I=10\text{S/A}$, $A_{V_t}=5\text{mV}\cdot\mu\text{m}$, $A_\beta=1\%\cdot\mu\text{m}$

$$\sigma_{\Delta I/I} = \sigma_u = \sqrt{(10 \cdot 0.005)^2 + (0.01)^2} = \sqrt{(5\%)^2 + (1\%)^2} \approx 5.1\%$$

- Mismatch is usually dominated by V_t mismatch.

How to Reduce Random Mismatch

- Use larger transistors with bigger W and bigger L
 - Larger area ☹️
 - Larger parasitics ☹️
- Reduce g_m/I
 - Bias in strong inversion $\rightarrow$ large V_{ov} $\rightarrow$ reduced output swing ☹️
- Reduce A_{vt} and A_β
 - Better process $\rightarrow$ increased cost ☹️

DAC INL/DNL Analysis

- Question to ask:
 - Given σ_u , how large are DAC INL and DNL?
 - It depends on different architectures
 - Thermometer DAC
 - Binary-weighted DAC
 - Segmented DAC

Thermometer DAC DNL Analysis

- For thermometer DAC, the step size for code k equals the magnitude of the k-th current source.

$$\text{DNL}[k] = \frac{\text{Step}[k] - \text{Step}_{\text{avg}}}{\text{Step}_{\text{avg}}} \approx \frac{I_k - I}{I} \approx \frac{\Delta I}{I}$$

$$\Rightarrow \sigma_{\text{DNL}[k]} = \sigma_{\Delta I/I} = \sigma_u$$

Thermometer DAC DNL Yield

- Question to ask:
 - We have a 8-bit thermometer DAC with $\sigma_u = 1\%$. We want the DAC DNL to be within ± 0.03 LSB. What is the yield after fabrication?
- Analysis
 - ± 0.03 LSB = $\pm 3\% = \pm 3\sigma_u$
 - For one code, its width falls in between $\pm 3\sigma$ is 99.73%, according to normal distribution.
 - We want all $2^8=256$ codes satisfy the requirement, thus, the yield is: $(99.73\%)^{256} \approx 50\%$
- How about a 12-bit DAC?
 - All 4096 codes satisfy the requirement $\rightarrow$ yield = $(99.73\%)^{4096} \approx 0$
 - Let us relax the DNL requirement to ± 0.05 LSB $\rightarrow$ yield $\approx 99\%$
 - A big change, why?

Thermometer DAC INL Analysis

$$\text{INL}[k] = \frac{I_{\text{out}}[k] - I_0[k]}{\text{Step}_{\text{avg}}} = \frac{\sum_{j=1}^k I_j - \frac{k}{N} \sum_{j=1}^N I_j}{\frac{1}{N} \sum_{j=1}^N I_j} = N \frac{\sum_{j=1}^k I_j}{\sum_{j=1}^N I_j} - k = N \frac{X}{Y} - k$$

$$\Rightarrow \text{var}[\text{INL}[k]] = \text{var} \left[N \frac{X}{Y} - k \right] = N^2 \text{var} \left[\frac{X}{Y} \right]$$


$$\frac{X}{Y} = \frac{\mu_X + \Delta X}{\mu_Y + \Delta Y} \approx \frac{\mu_X}{\mu_Y} + \frac{\Delta X}{\mu_Y} - \frac{\mu_X \Delta Y}{\mu_Y^2}$$

$$\text{var} \left[\frac{X}{Y} \right] \approx \left(\frac{\mu_X}{\mu_Y} \right)^2 \left(\frac{\sigma_X^2}{\mu_X^2} + \frac{\sigma_Y^2}{\mu_Y^2} - 2 \frac{\text{cov}(X, Y)}{\mu_X \mu_Y} \right)$$

$$\text{var}[\text{INL}[k]] \approx k(1 - k/N) \sigma_u^2$$

$$\sigma_{\text{INL}}[k] \approx \sigma_u \sqrt{k(1 - k/N)}$$

Thermometer DAC σ_{INL} Plot

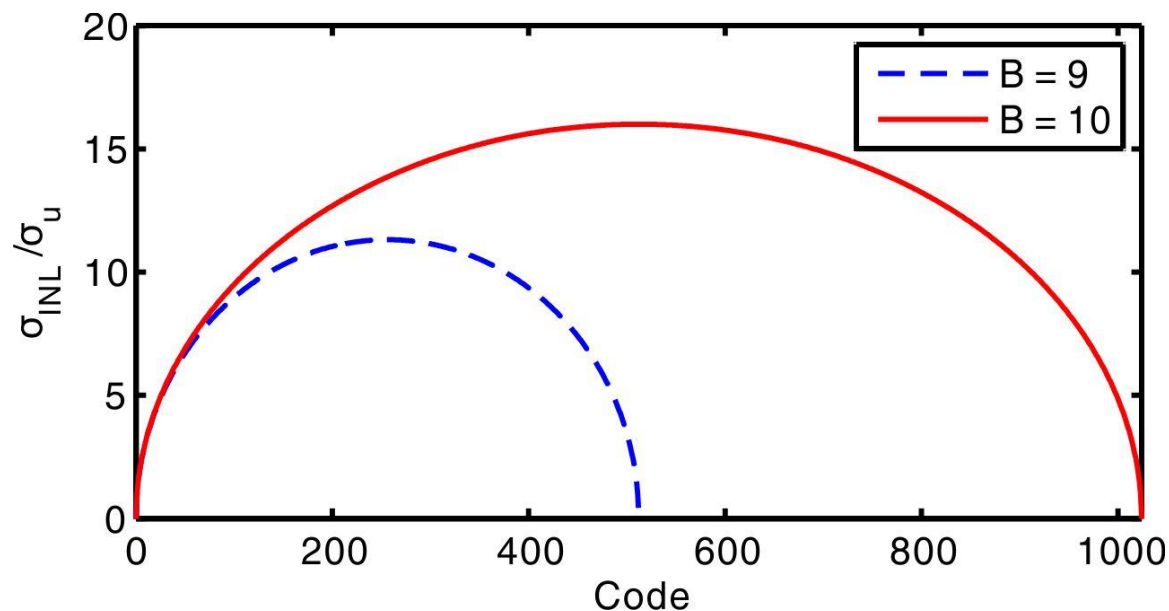


- σ_{INL} is maximum at mid-scale ($k=N/2=2^{B-1}$)

$$\sigma_{\text{INL}}[N/2] \approx \sigma_u \sqrt{\frac{N}{2} \left(1 - \frac{N/2}{N}\right)} = \frac{\sigma_u}{2} \sqrt{N} \approx \sigma_u 2^{B/2-1}$$


- This is a “Brownian bridge:” summation of random DNLs
- Unlike σ_{DNL} , σ_{INL} grows as B increases.

Thermometer DAC INL

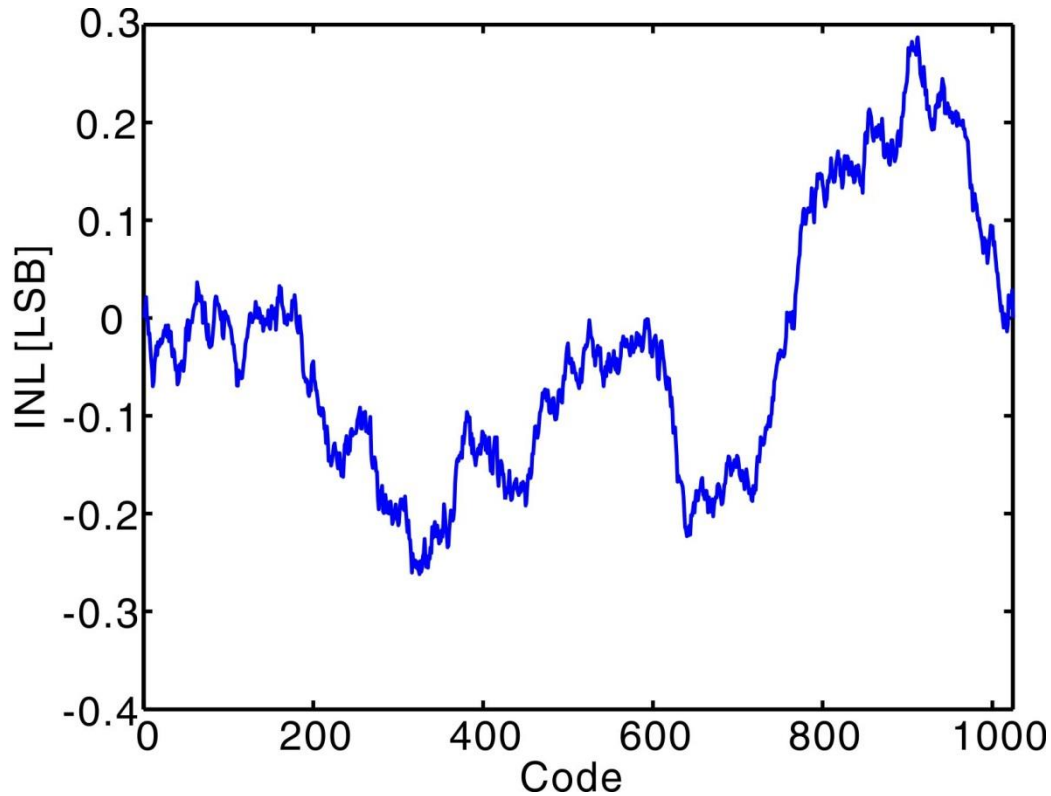

- 1 run for a 10-b DAC with $\sigma_u=1\%$

Thermometer DAC σ_{INL} Plot

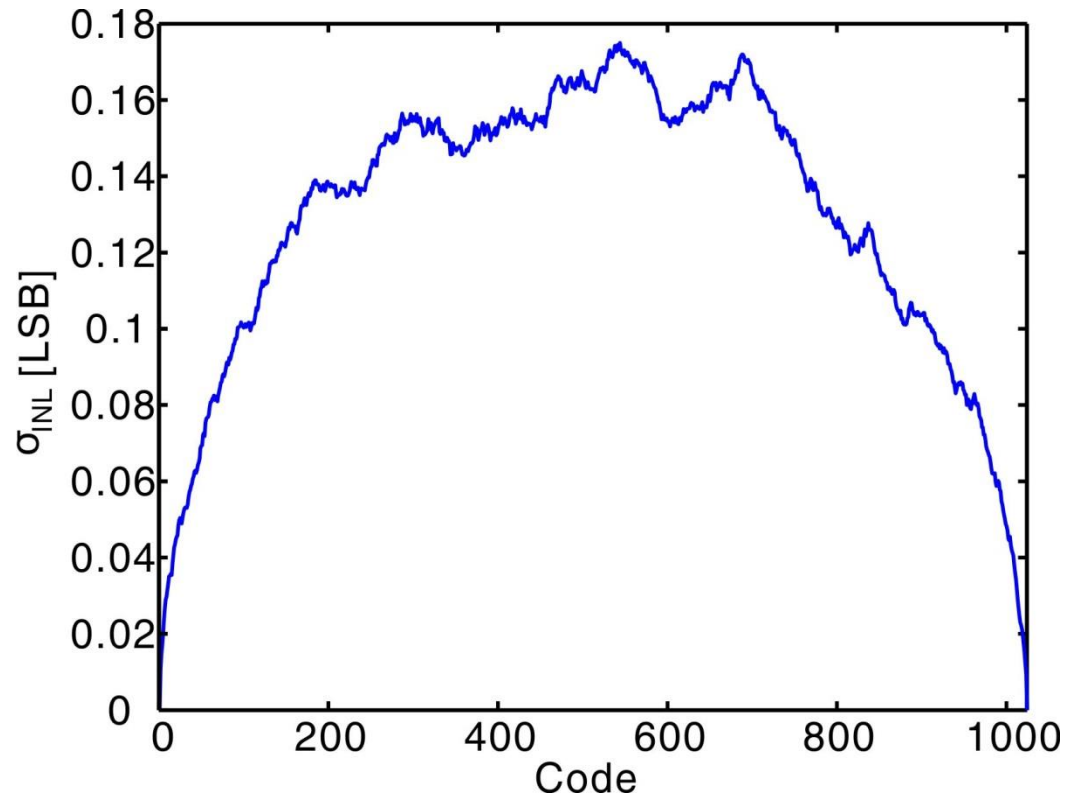

- 100 runs, plot σ_{INL}
- Match well with theory

Thermometer DAC INL Yield

- Question to ask:
 - We have a 8-bit thermometer DAC with $\sigma_u = 1\%$. We want the DAC INL to be within ± 0.03 LSB. What is the yield after fabrication?
 - It turns out that this is not easy to solve analytically
 - Unlike $\{DNL[k]\}$, $\{INL[k]\}$ are not independent
- In general, DAC designers will rely on numerical Monte Carlo simulations to estimate the DNL/INL yield instead of solving analytical solutions
 - This method is conceptually very simple
 - It works for all types of DACs (thermometer, binary, and segmented)
 - Yet a basic understanding will be very helpful for finding errors in the simulation

Binary Weighted DAC DNL Analysis

- $\{DNL[k]\}$ are different and depend on transition
- Worst case: 01111111 ... $\rightarrow$ 1000000 ...
 - Turning off all LSBs and turn on the MSB


$$\text{Step}[2^{B-1}] = \sum_{i=2^{B-1}}^{2^B-1} I_i - \sum_{j=1}^{2^{B-1}-1} I_j$$

$$DNL[2^{B-1}] = \frac{\text{Step}[2^{B-1}] - \text{Step}_{\text{avg}}}{\text{Step}_{\text{avg}}} \approx \sum_{i=2^{B-1}}^{2^B-1} \frac{\Delta I_i}{I} - \sum_{j=1}^{2^{B-1}-1} \frac{\Delta I_j}{I}$$

$$\sigma_{DNL, \text{worst}}^2 = (2^{B-1}) \sigma_u^2 + (2^{B-1} - 1) \sigma_u^2 = (2^B - 1) \sigma_u^2$$


- For example, $B = 10$, $\sigma_u = 1\% \rightarrow \sigma_{DNL, \text{worst}} = 0.32 \text{ LSB}$
 - Much larger than that of the thermometer DAC ($\sigma_{DNL} = 0.01 \text{ LSB}$).

Binary Weighted DAC DNL

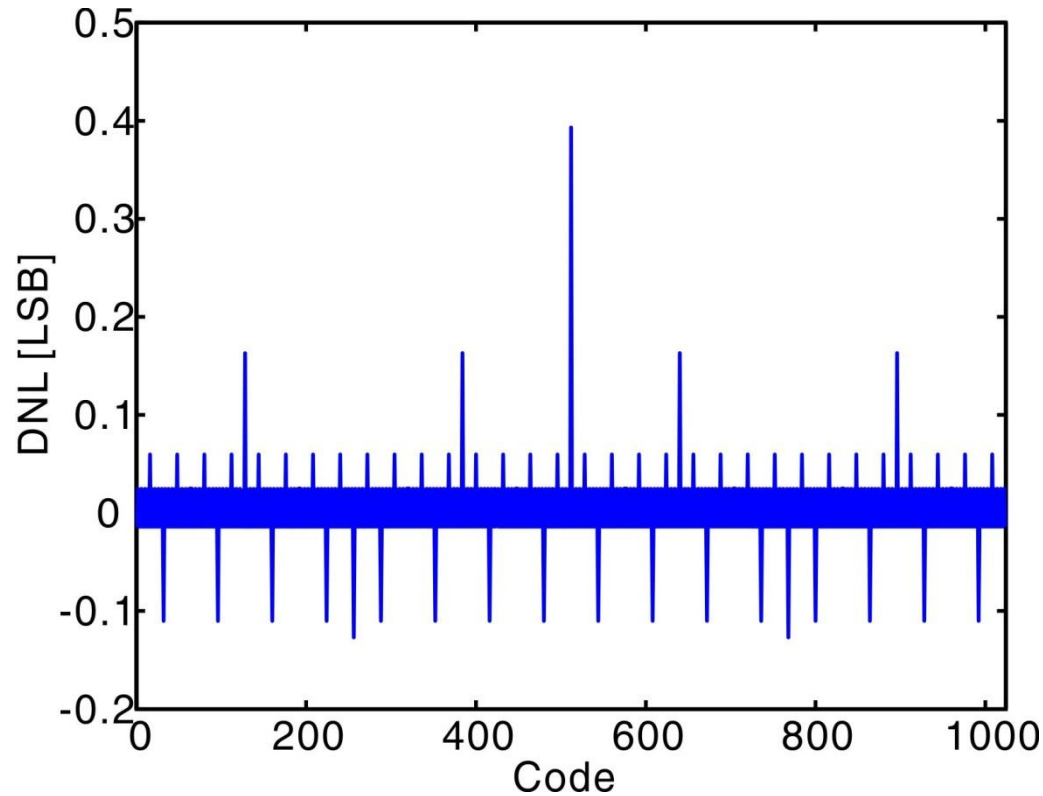


- 1 run for a 10-b DAC with $\sigma_u=1\%$

Binary Weighted DAC DNL

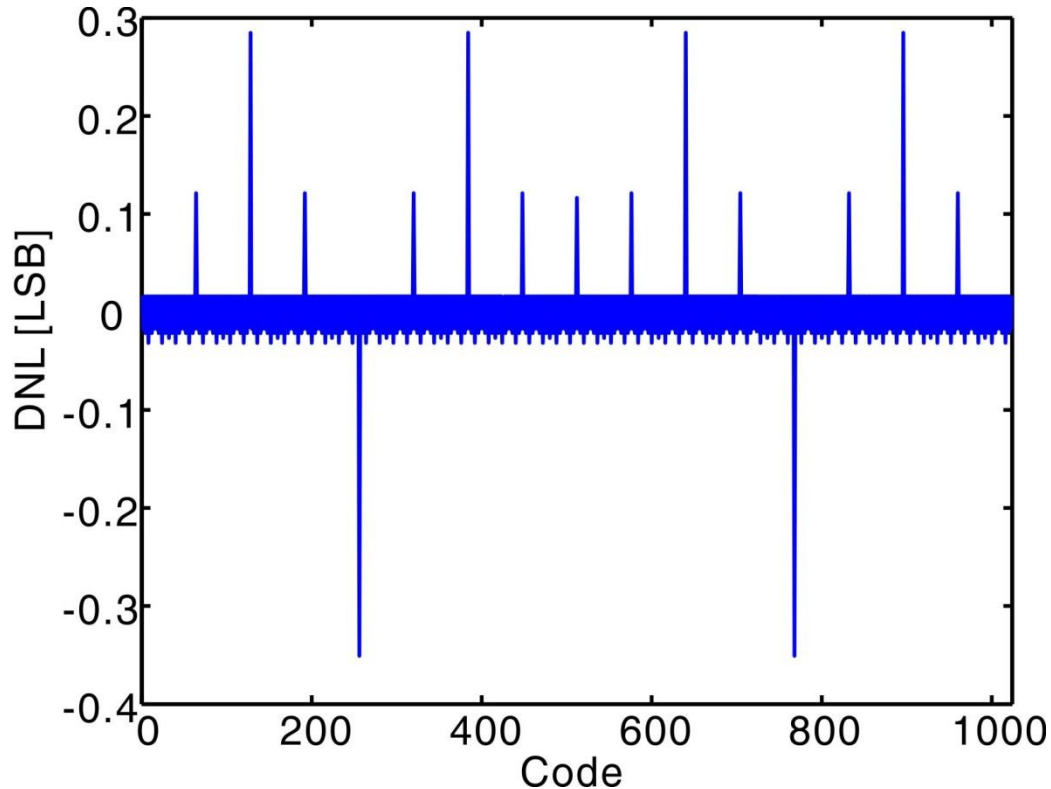

- Another run, worst DNL does not happen at the MSB transition
 - Due to randomness

Binary Weighted DAC σ_{DNL}

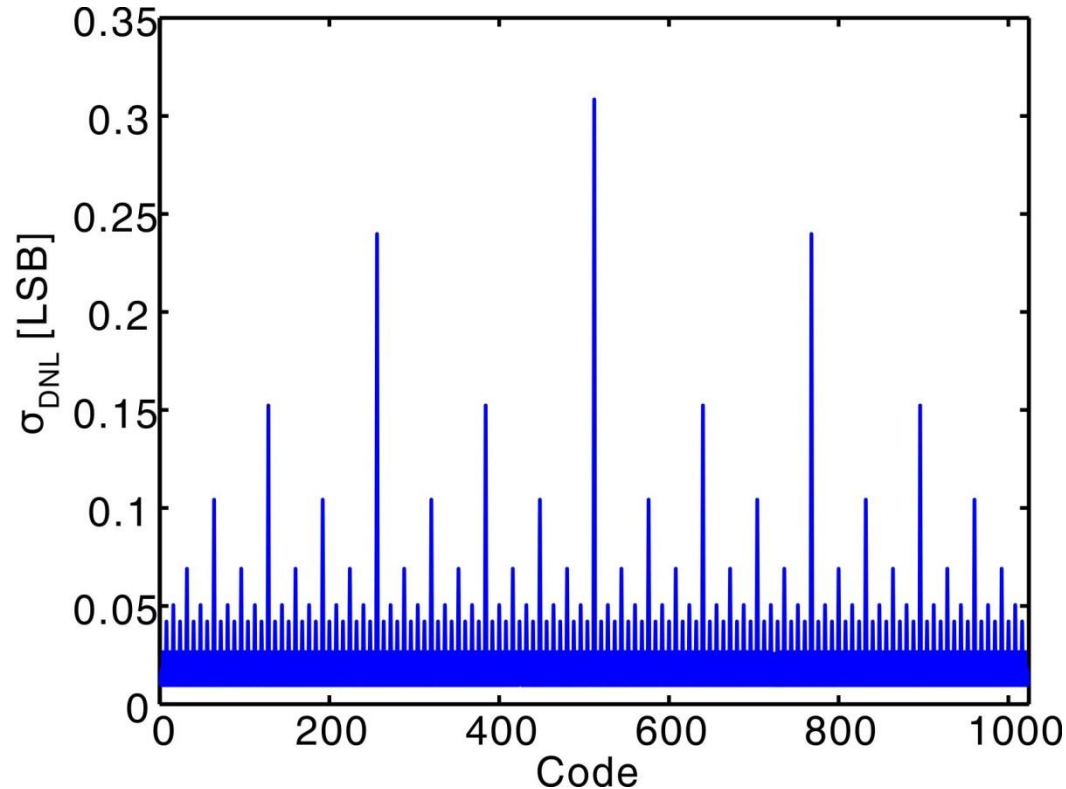

- 100 runs, plot σ_{DNL}
- Match well with theory

Binary Weighted DAC INL Analysis


- σ_{INL} is the same as that for a thermometer DAC
 - Why?
 - INL is the overall deviation from the ideal straight line
 - It does not matter how we select the elements

$$\text{INL}[k] = \frac{I_{\text{out}}[k] - I_0[k]}{\text{Step}_{\text{avg}}}$$

$$\sigma_{\text{INL}}[k] \approx \sigma_u \sqrt{k(1 - k/N)}$$


- What is the difference in the INL of a binary weighted DAC?
 - There are large discontinuities due to large DNLs

Binary Weighted DAC INL

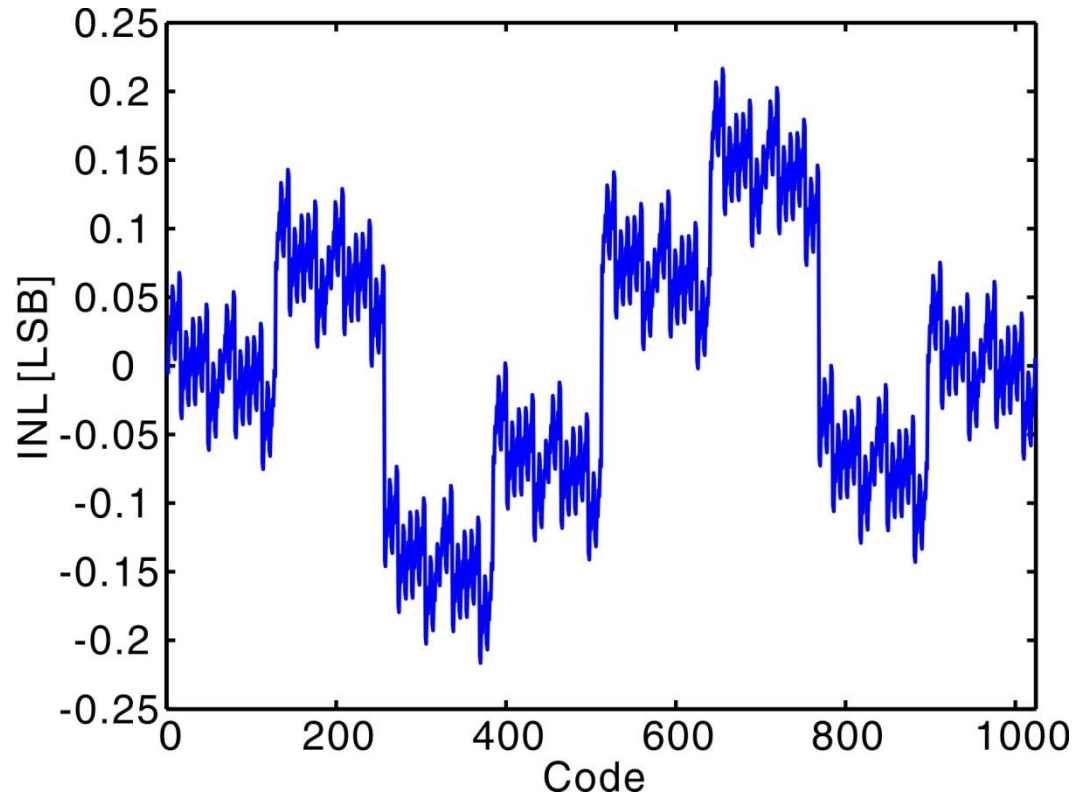

- 1 run for a 10-b DAC with $\sigma_u=1\%$

Binary Weighted DAC σ_{INL} Plot

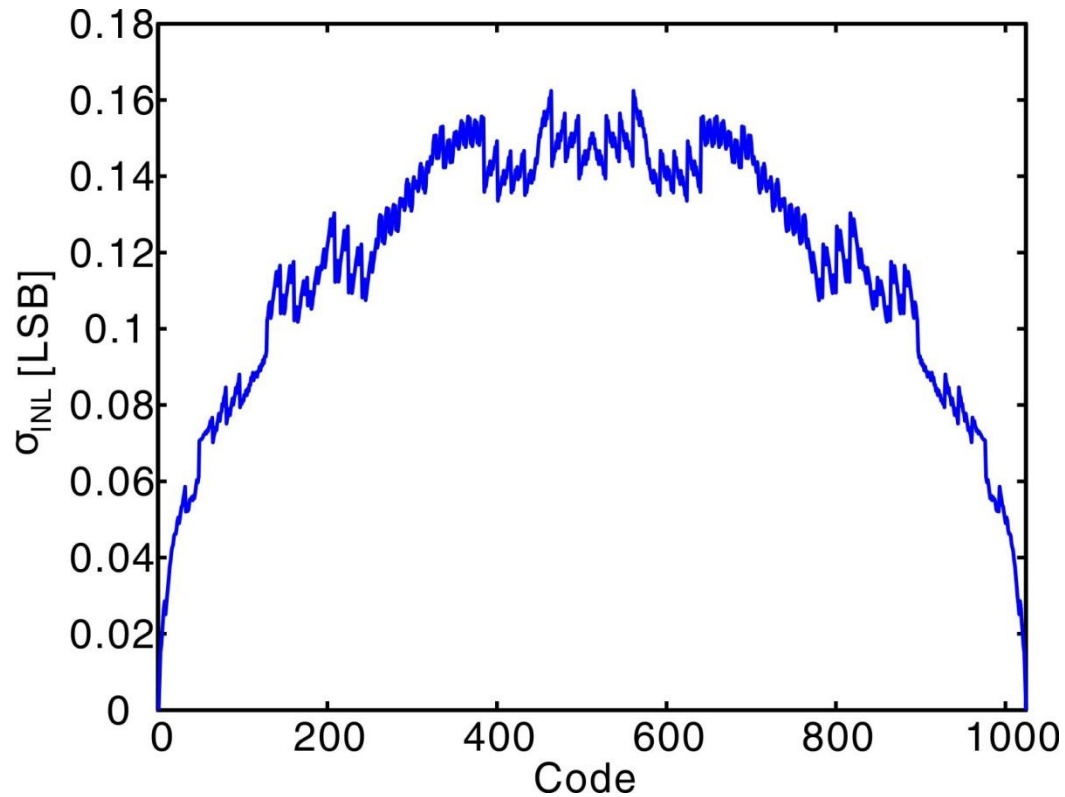


- 100 runs, plot σ_{INL}
- Match well with theory

Segmented DAC DNL/INL Analysis


- Worst case DNL
 - When all LSB DAC elements turn off and 1 MSB DAC element turns on
 - Same DNL as a binary weighted DAC with B_b+1 bits
- INL
 - σ_{INL} is the same as that of thermometer DAC

Segmented DAC DNL

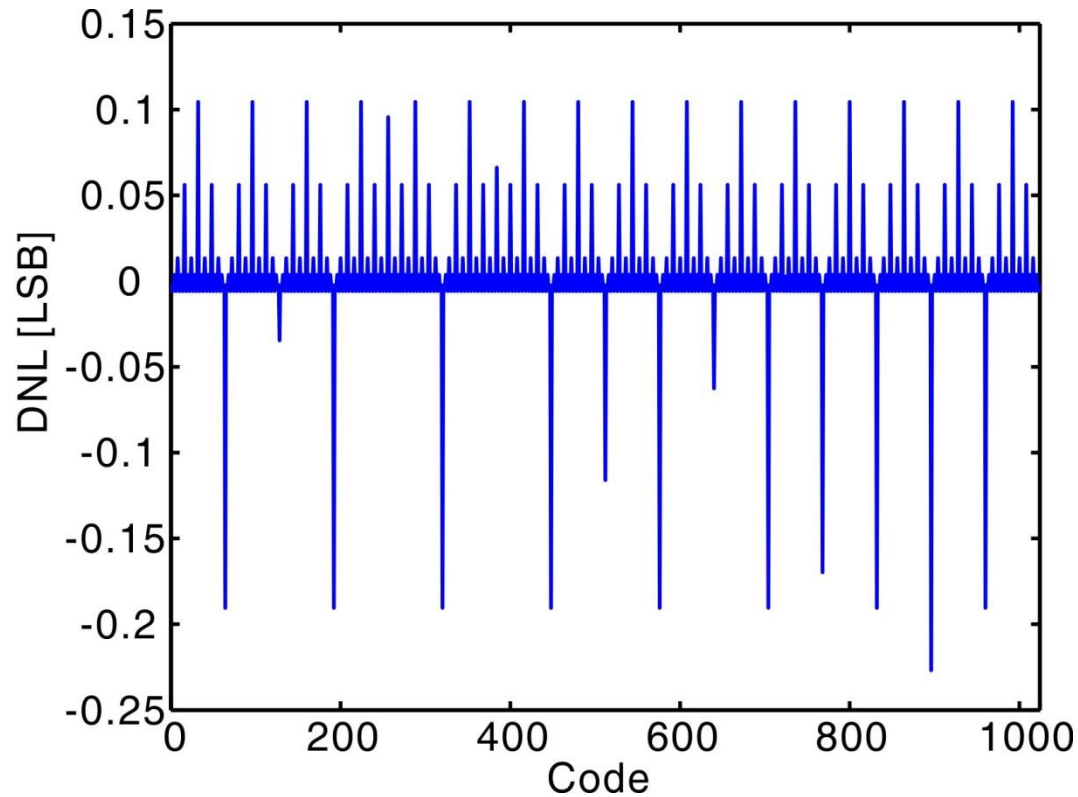


- 1 run for a 10-b segmented DAC (3b MSB and 7b LSB) with $\sigma_u=1\%$

Segmented DAC σ_{DNL} Plot

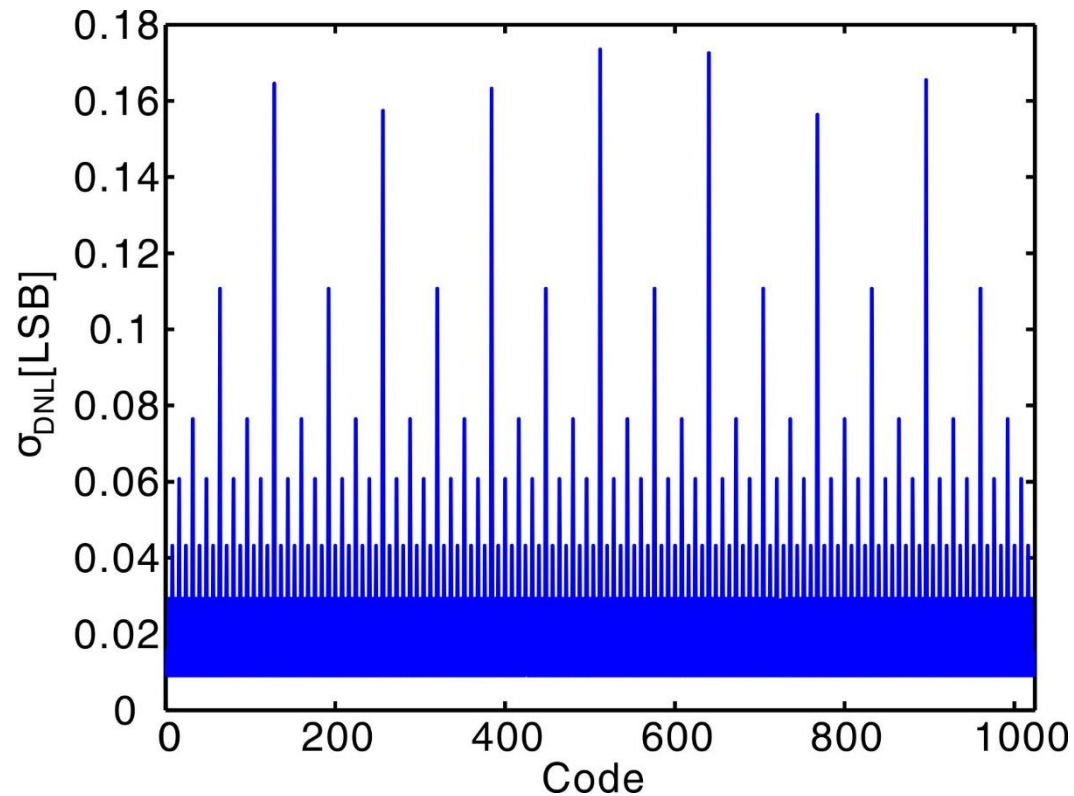


- 100 runs, plot σ_{DNL}
- Match well with theory

Segmented DAC INL

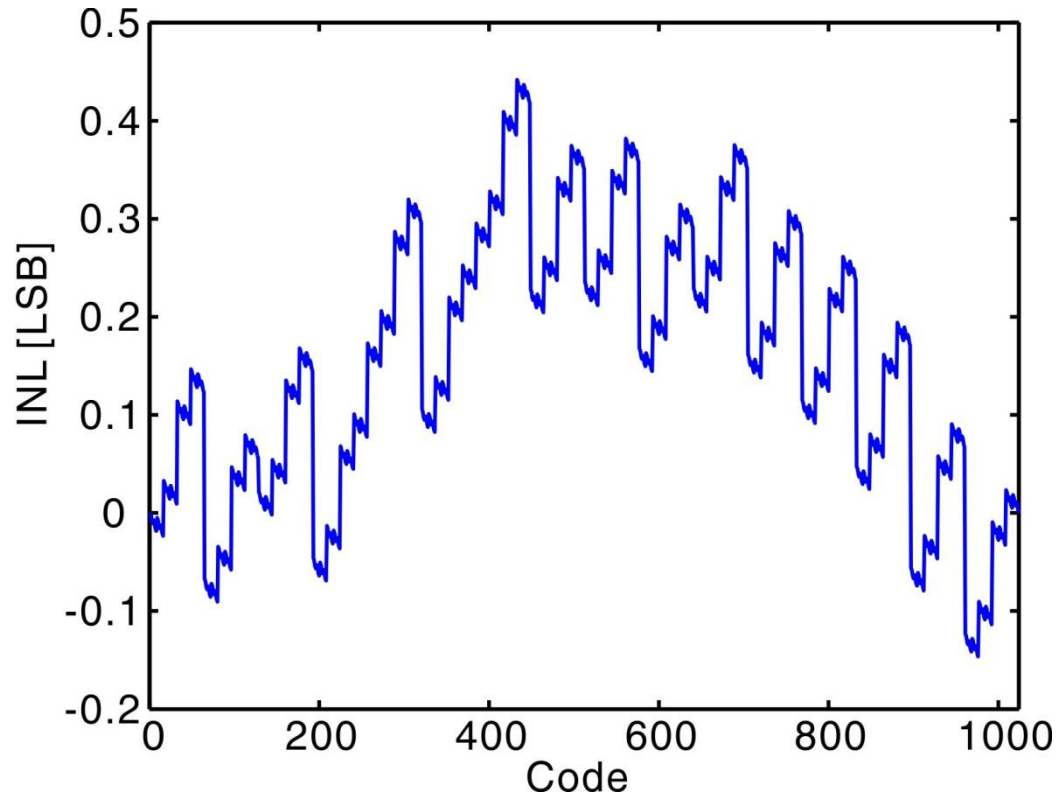

- 1 run for a 10-b segmented DAC (3b MSB and 7b LSB) with $\sigma_u=1\%$

Segmented DAC σ_{INL} Plot

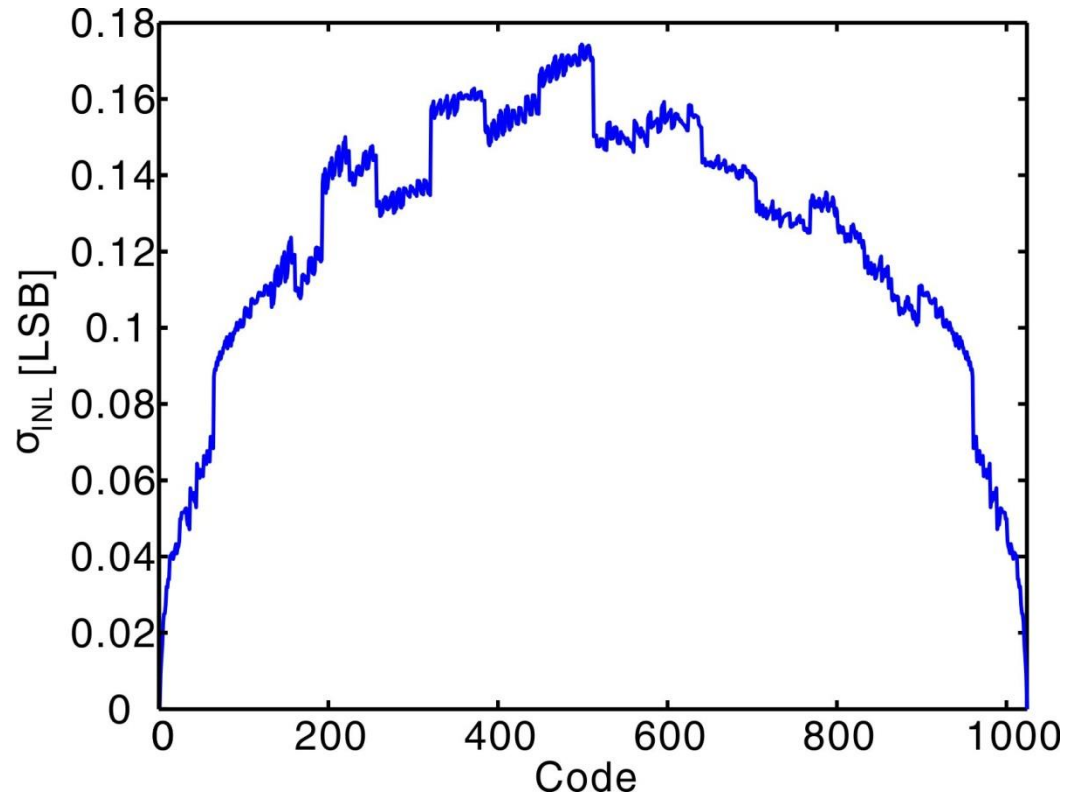

- 100 runs, plot σ_{INL}
- Match well with theory

Summary


	Thermometer	Segmented	Binary Weighted
σ_{INL}	$\sigma_{\text{INL}}[k] \approx \sigma_u \sqrt{k(1 - k/N)}$		
σ_{DNL} (worst case)	σ_u	$2^{(B_b+1)/2} \sigma_u$	$2^{B/2} \sigma_u$
# elements	$2^B - 1$	$B_b + 2^{B_t} - 1$	B

Segmented DAC in general achieves the best trade off.

- Most high-performance DACs adopt segmented DAC structure.

Finite Output Impedance

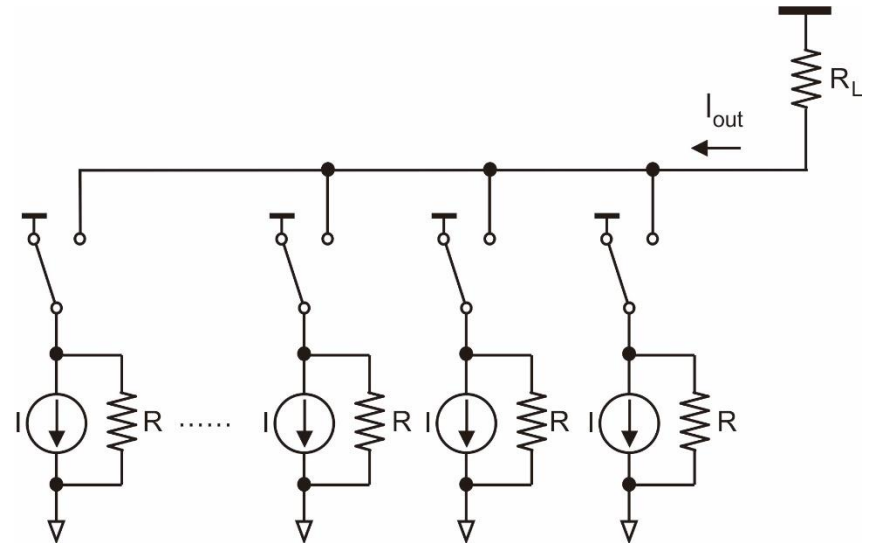- Current source with finite output resistance R
- The number of closed switches:
$$2^B \times \frac{D_{in}}{FS}$$
- $$V_{out} = 2^B \times \frac{D_{in}}{FS} \times (R_L \parallel \frac{R}{2^B \times \frac{D_{in}}{FS}})$$
- As D_{in} increases, do the code widths get wider or narrower?
- Need to make R large enough
 - Cascode
 - Source degeneration



Overview

- Topologies
- Current steering DAC architectures
- Static errors
- **Dynamic errors**
- Example implementations

Dynamic DAC Errors


- Dynamic DAC errors are generally hard to model
 - DAC output is continuous in time, and thus, any error at any time instance causes trouble!
 - High-performance DAC design is nontrivial.
- Glitches due to timing errors
 - Current sources do not switch simultaneously
- Clock feedthrough
 - Coupling from switch signals to DAC output
- Finite settling time and slewing
 - Finite RC time constant
 - Signal dependent slewing
- Inter symbol interference
 - Unmatched rising and falling edges

Useful References

- Doris, van Roermund, Leenaerts, Wide-Bandwidth High Dynamic Range D/A Converters, Springer, 2006.
- Bosch, Steyaert, Sansen, Static and Dynamic Performance Limitations for High Speed D/A Converters, Kluwer, 2004.
- Gustavsson, Chapter 12
- M. Albiol, J.L. Gonzalez, E. Alarcon, "Mismatch and dynamic modeling of current sources in current-steering CMOS D/A converters," IEEE TCAS I, pp. 159-169, Jan. 2004
- T. Chen and G.G.E. Gielen, "The analysis and improvement of a current-steering DAC's dynamic SFDR," IEEE Trans. Ckts. Syst. I, pp. 3-15, Jan. 2006.


Glitch Impulse Error

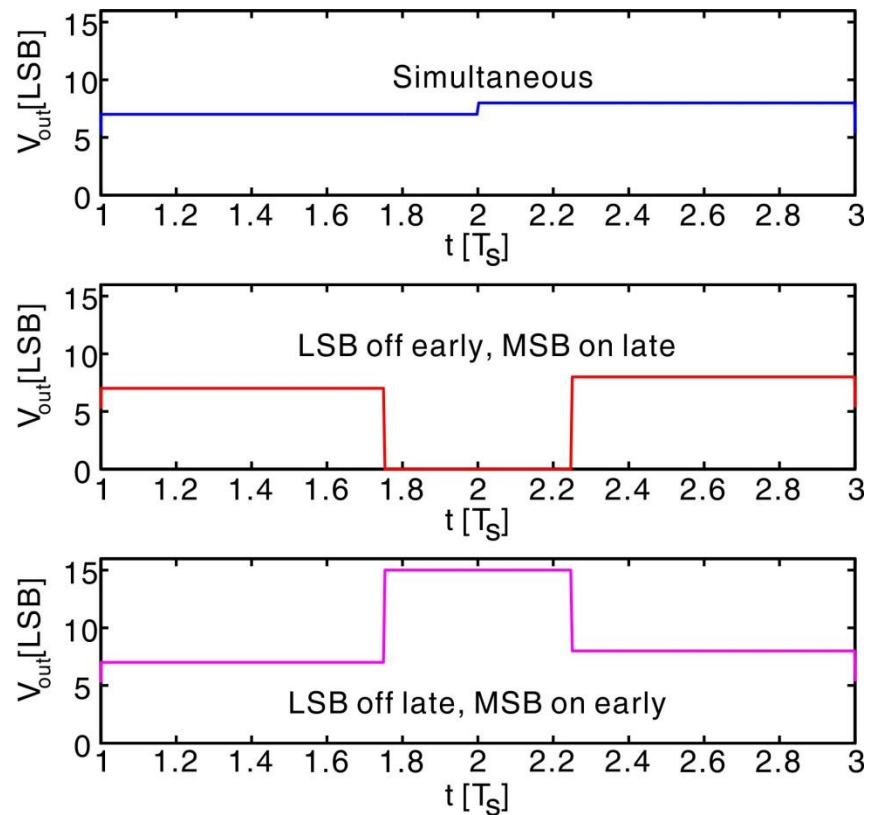- Current sources need to be turned on/off simultaneously
 - Consider binary weighted DAC transition $0111 \rightarrow 1000$
- Worst case glitch impulse area:
 $\propto \Delta t 2^{B-1}$
- LSB area: T_s
- $\Delta t 2^{B-1} \ll T_s \rightarrow \Delta t \ll T_s/2^{B-1}$
- E.g., $T_s = 1\text{ns}$, $B = 10$, $\Delta t < 2\text{ps}$
 - Using a segmented structure will help




Basic Differential Pair Switch

Single-ended

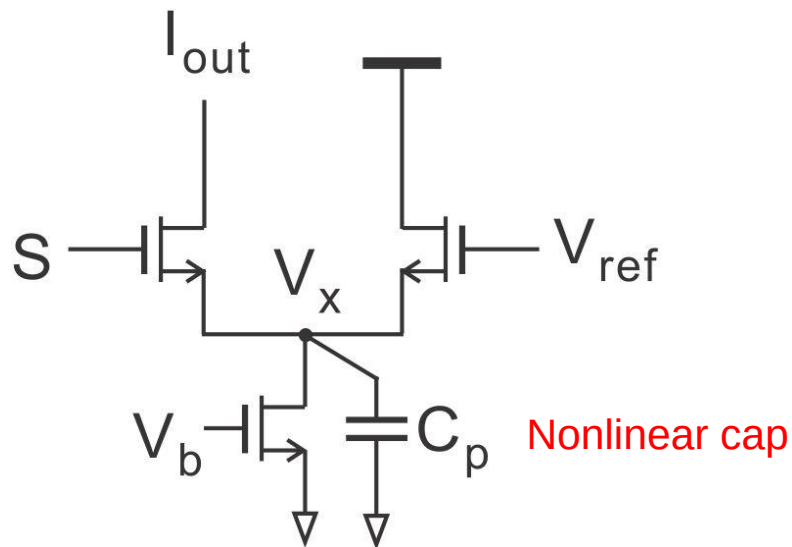

Differential


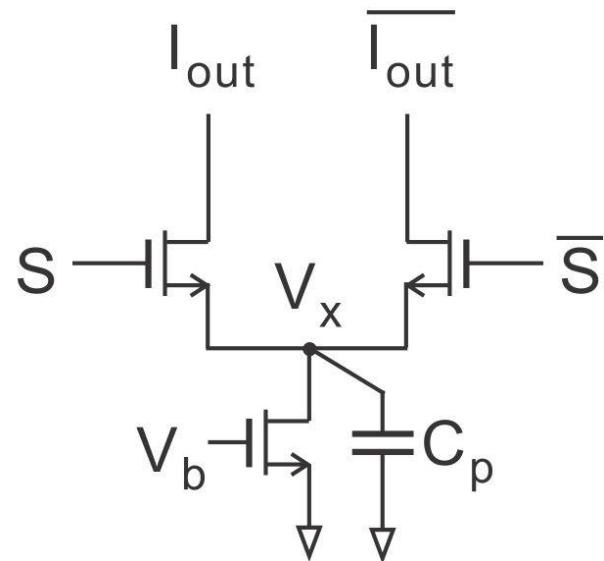


- For high-speed, never turn off the current source
 - Parasitic cap needs to be recharged
- Need to minimize the swing at V_x

Design Techniques



- Data retiming
 - Use a global clock to resample data near the current cells, so that they switch simultaneously independent of encoder delays
- Make before break
 - Ensure that the current is never turned off
 - S and S_bar are not simultaneously off
- Low swing driver
 - Drive differential pair with low swing to minimize coupling from control signals to output

Data Retiming

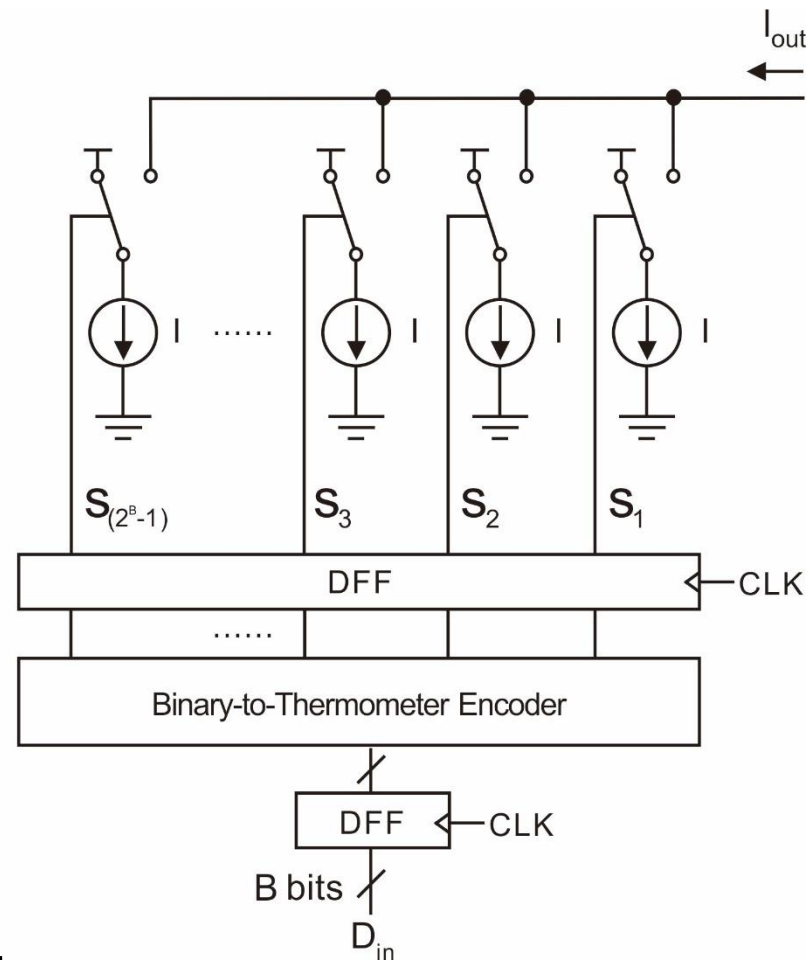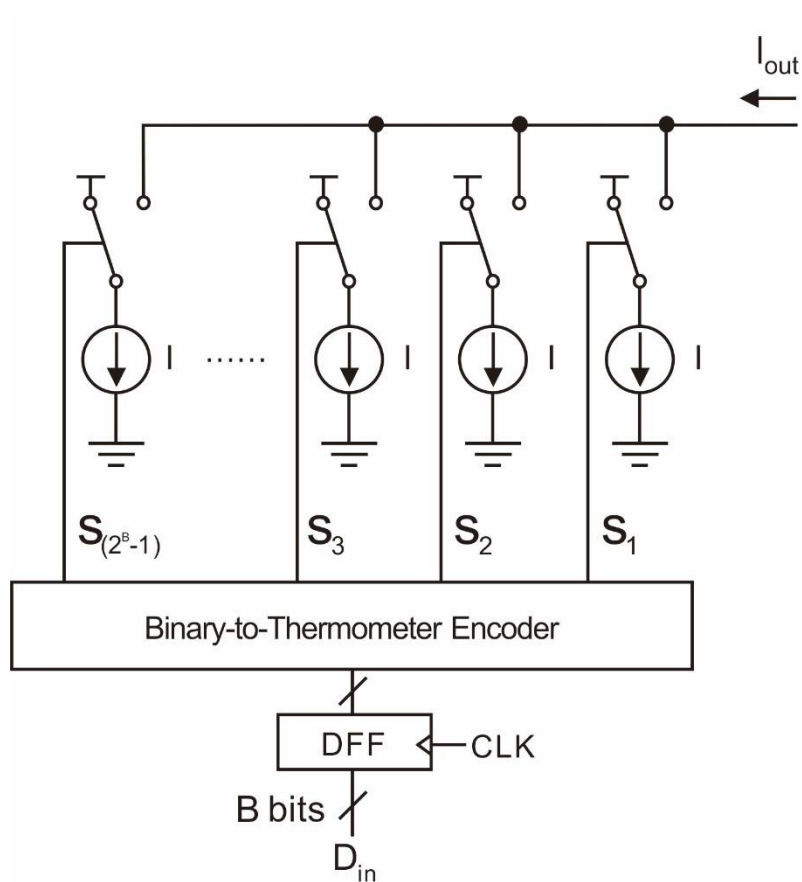


- Use a segmented DAC will help too.

Make Before Break

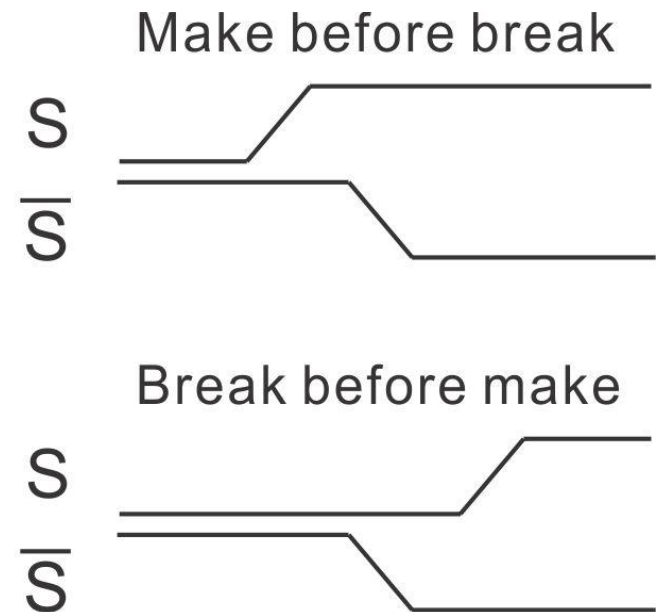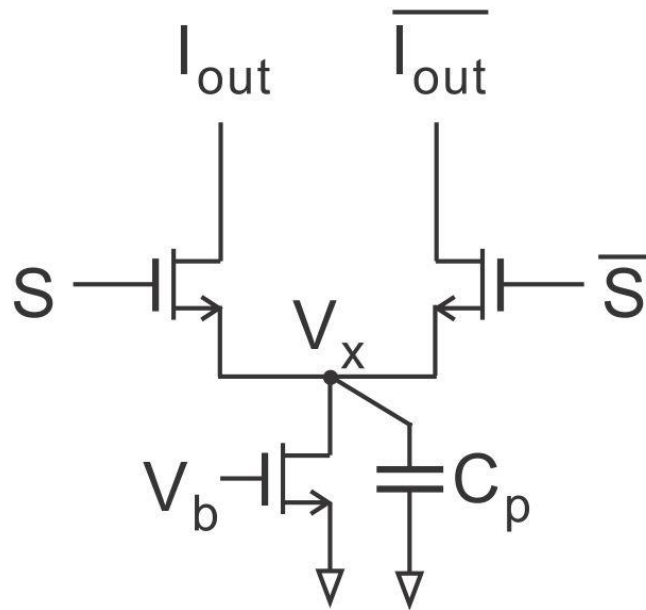

- Ensure that the current source is never turned off

Example Current Cell Implementation

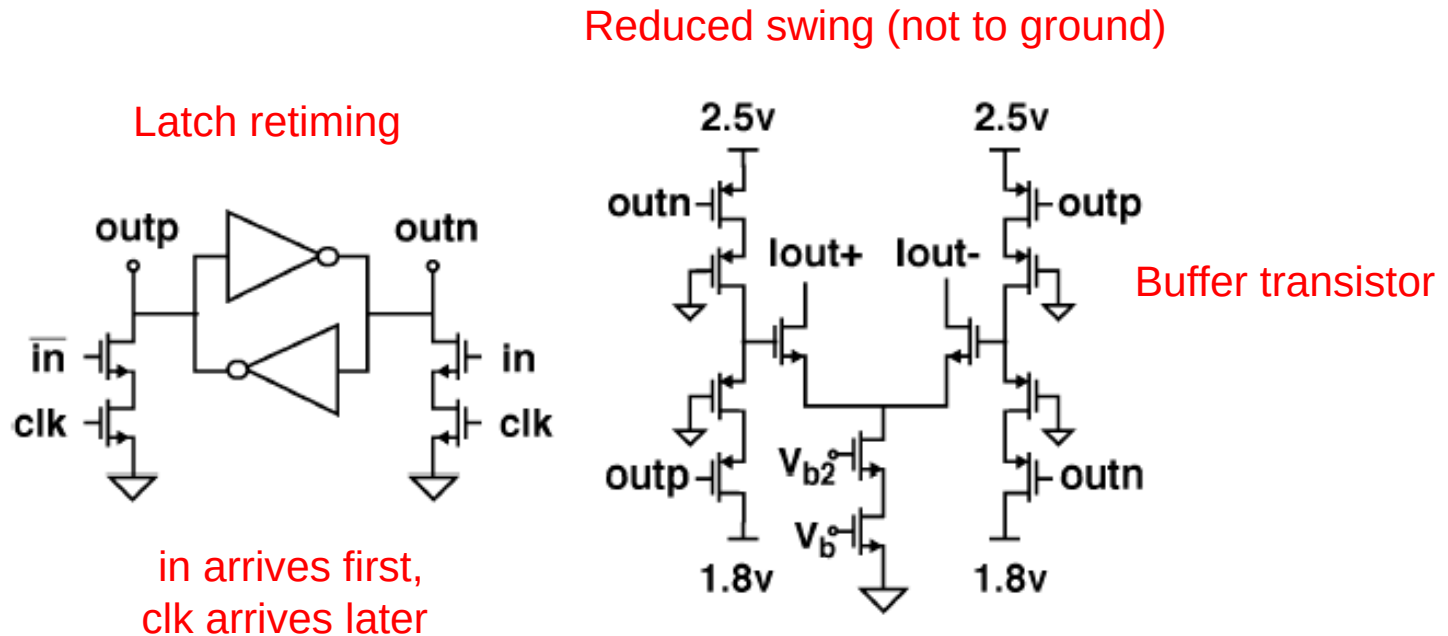

[Barkin & Wooley, JSSC 4/2004]

Overview

- Topologies
- Current steering DAC architectures
- Static errors
- Dynamic errors
- Example implementations

High Performance DAC Example #1

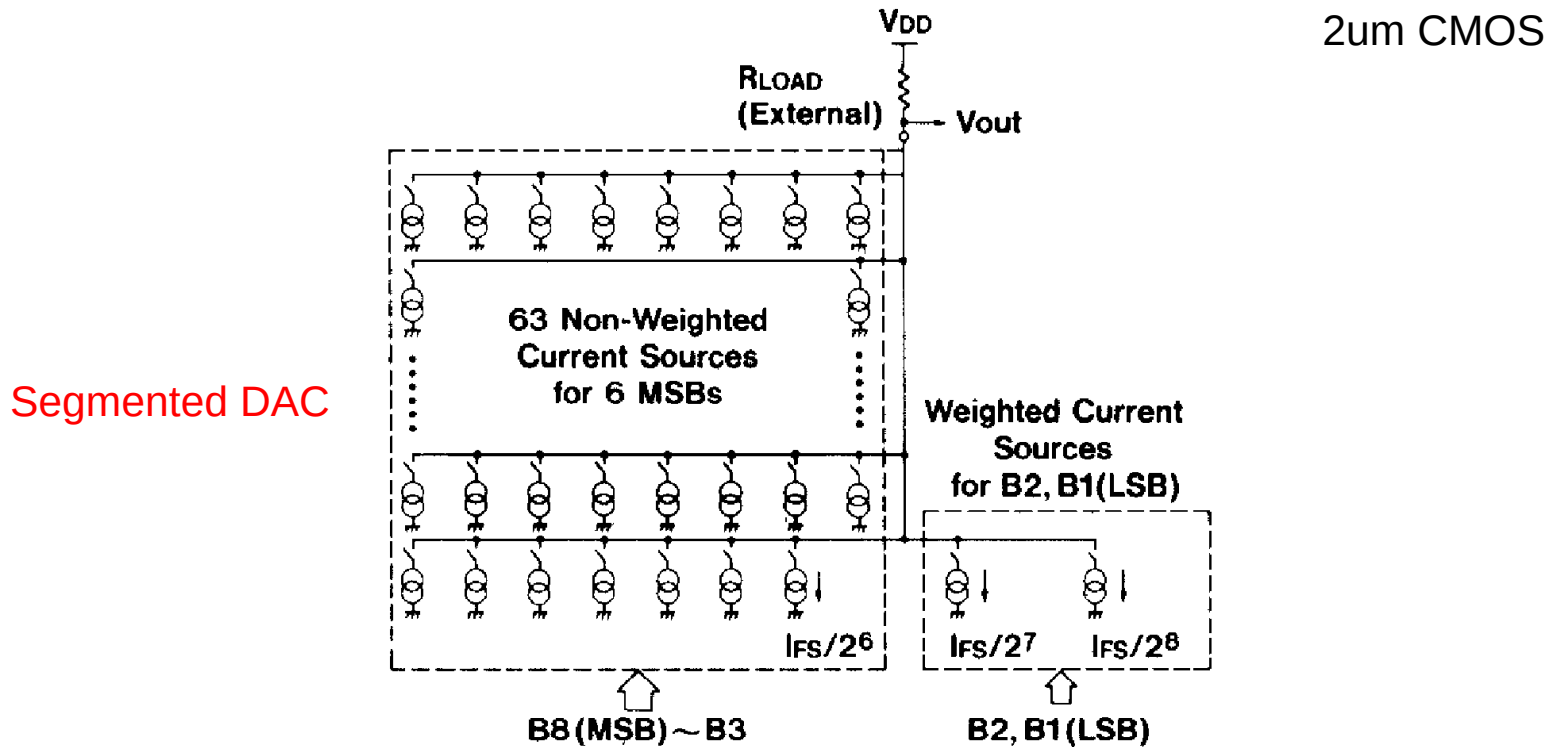


Fig. 1. Basic architecture of the DAC.

[T. Miki, Y. Nakamura, M. Nakaya, S. Asai, Y. Akasaka, and Y. Horiba, "An 80-MHz 8-bit CMOS D/A Converter," IEEE J. of Solid-State Circuits, pp. 983-988, Dec. 1986.]

Decoder Design

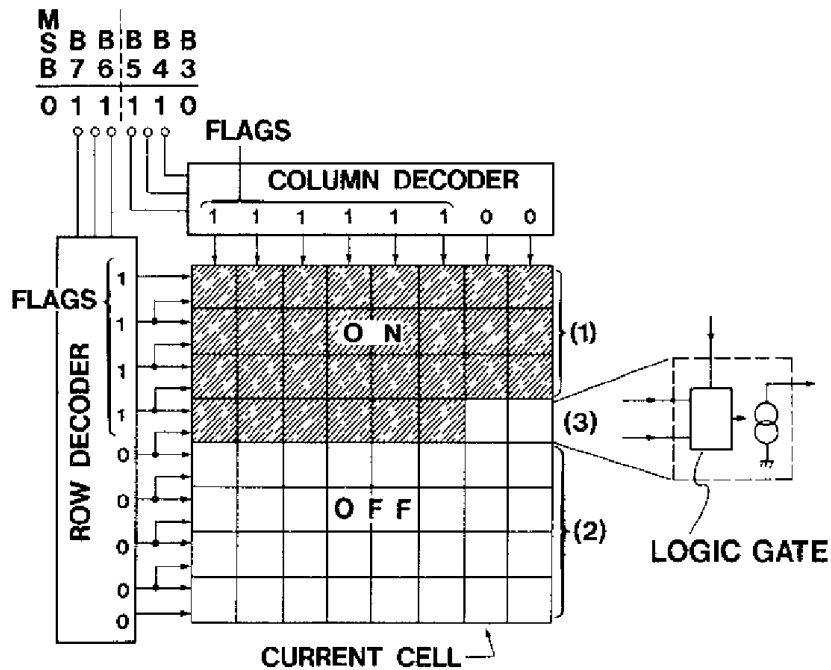


Fig. 2. Two-step decoding.

Fast decoding


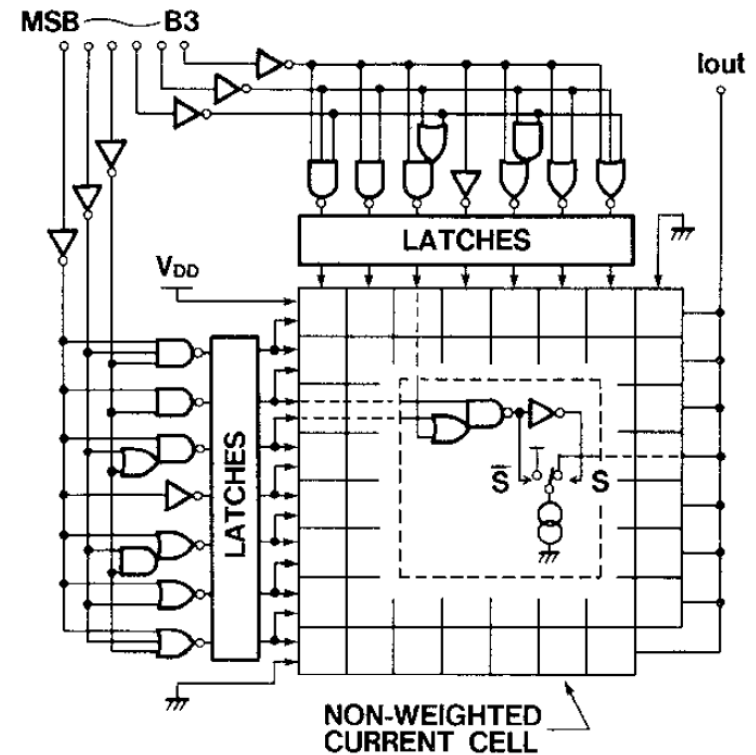
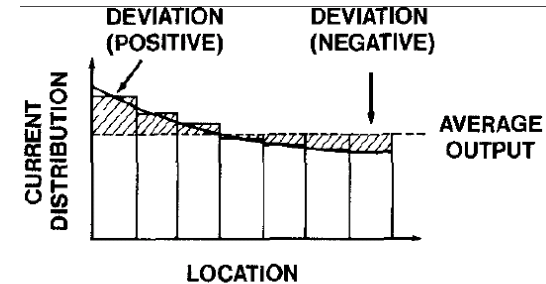


Fig. 3. High-speed decoding circuit.

Latch retiming

Mitigating IR Drop


Systematically decreasing currents

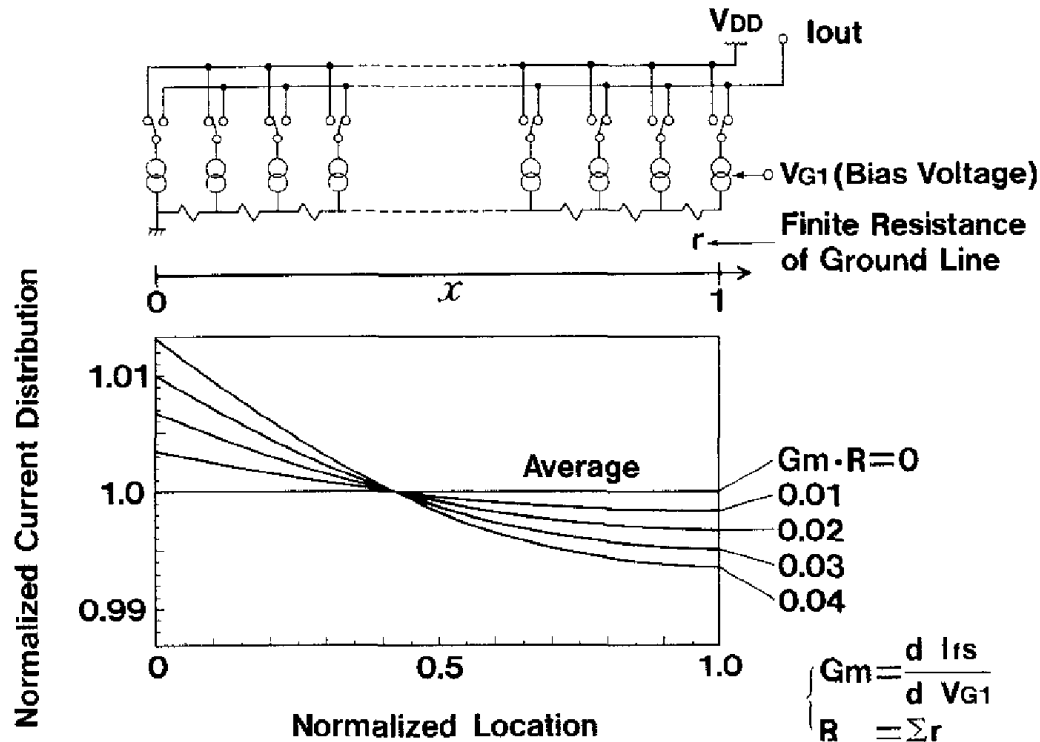

1	2	3	4	5	6	7
SEQUENTIAL SWITCHING						
6	4	2	1	3	5	7
SYMMETRICAL SWITCHING						


Reducing INL

Fig. 9. Symmetrical switching.

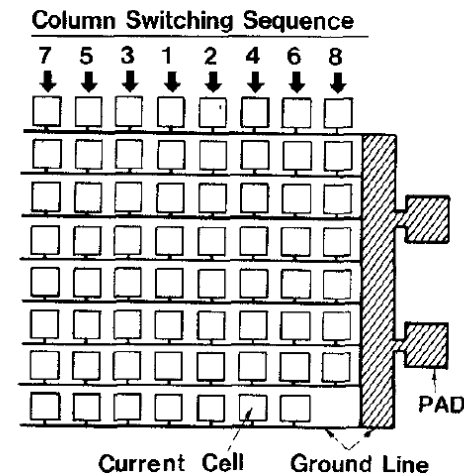

INL can be reduced by re-arranging DNLs

High Performance DAC Example #2

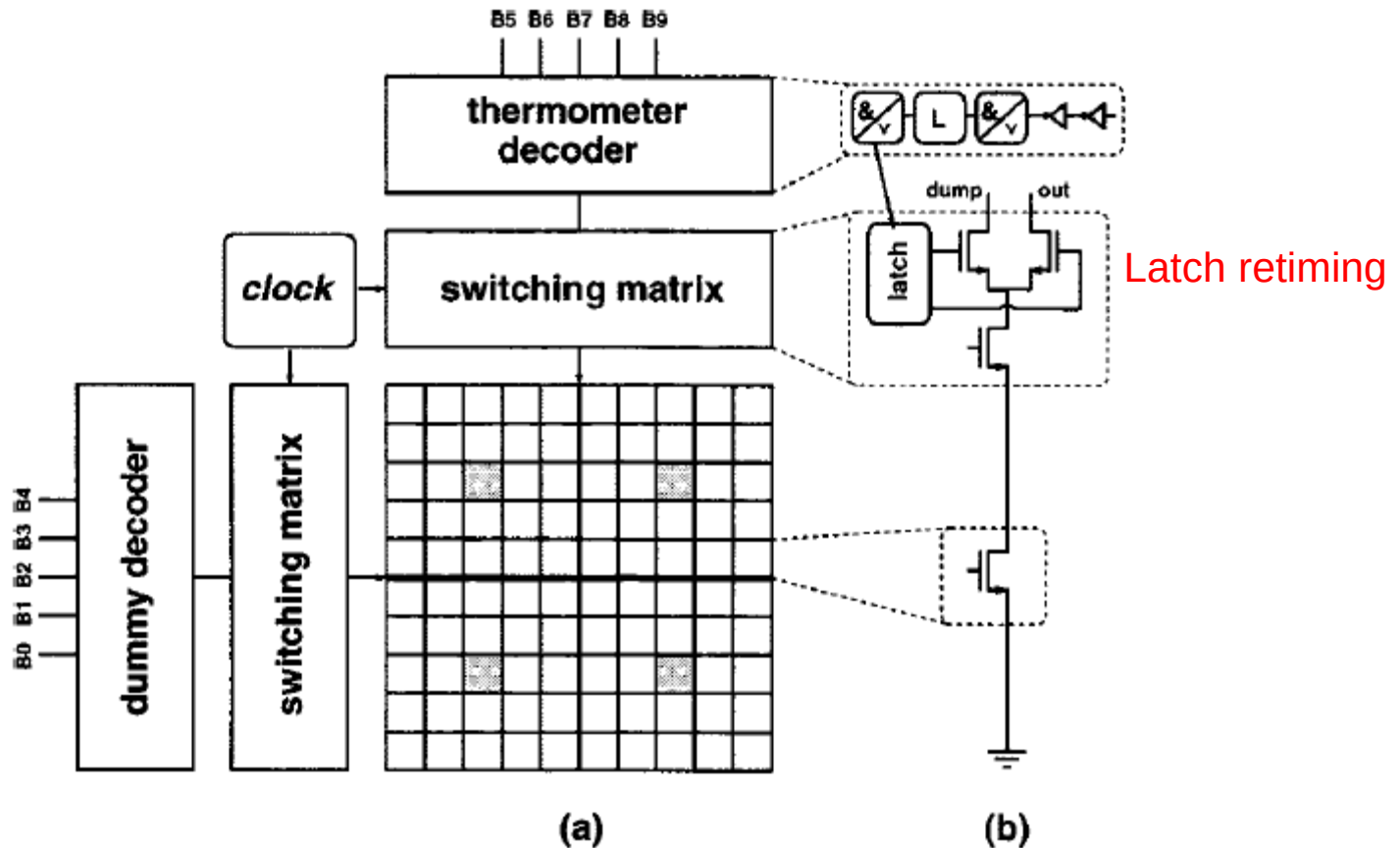


[Van den Bosch, JSSC 3/2001]



	Mo	B0				B0	B0				B0	Mo	
			16	14					14	16			
		8	4	2	6			6	2	4	8		
		5	1	3	7			7	3	1	5		
			13	15					15	13			
B3	B2					B1	B1					B4	
	B2					B1	B1					B4	
			13	15					15	13			
		5	1	3	7			7	3	1	5		
		8	4	2	6			6	2	4	8		
			16	14					14	16			
	Mo	B0				B0	B0				B0	Mo	

[Van den Bosch, JSSC 3/2001]



Measurements

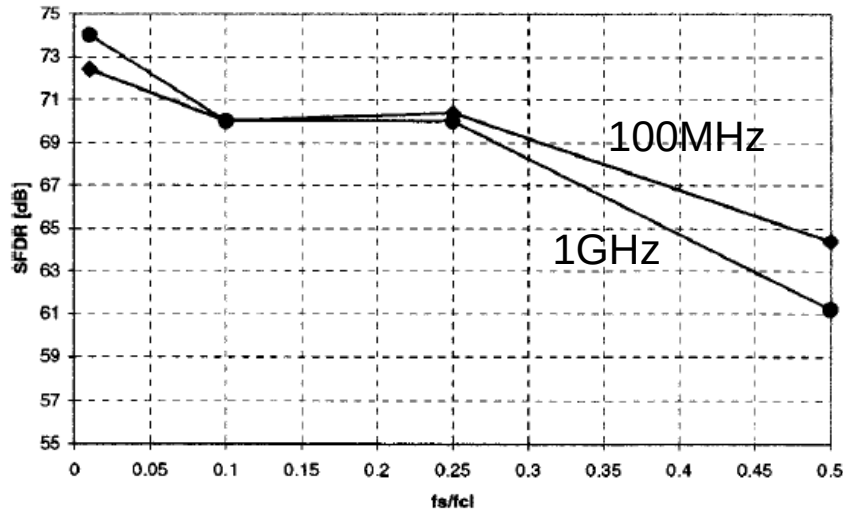


Resolution	10 bit
Update rate	Up to 1 GS/s
INL	< 0.2LSB
DNL	<0.15 LSB
SFDR (490MHz@1GS/s)	61.2 dB
Analog/digital voltage supply	3V / 1.9 V
Power consumption	110mW (490Mhz@1GHz)
Active area	0.35 mm ²
Process	0.35 μm CMOS

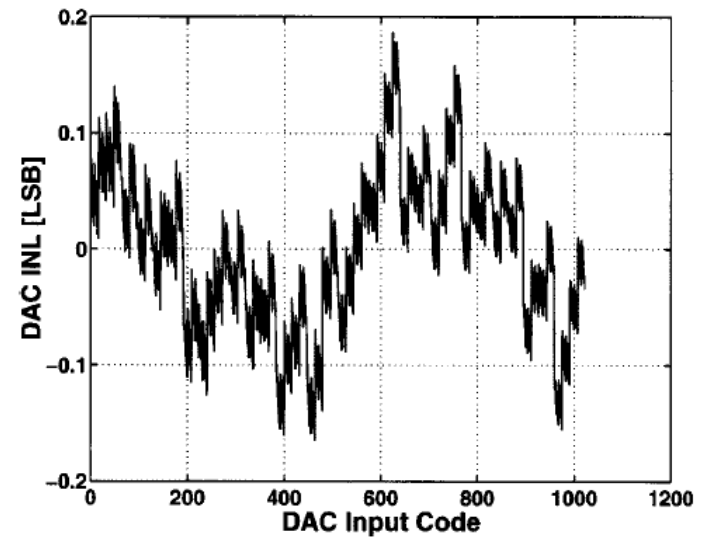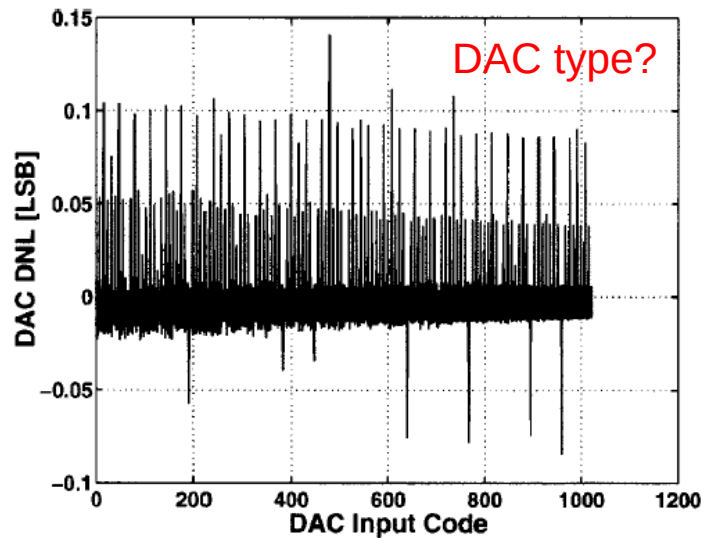

High Performance DAC Example #3

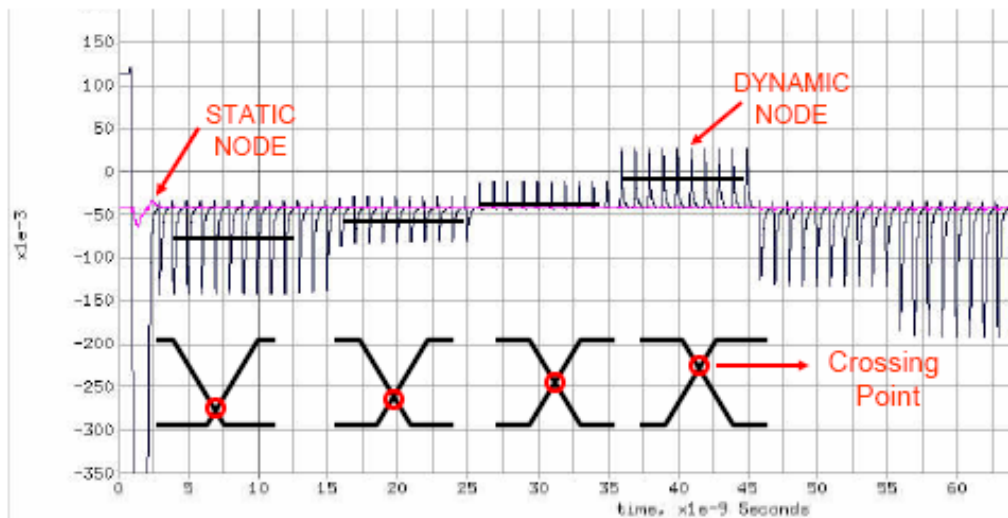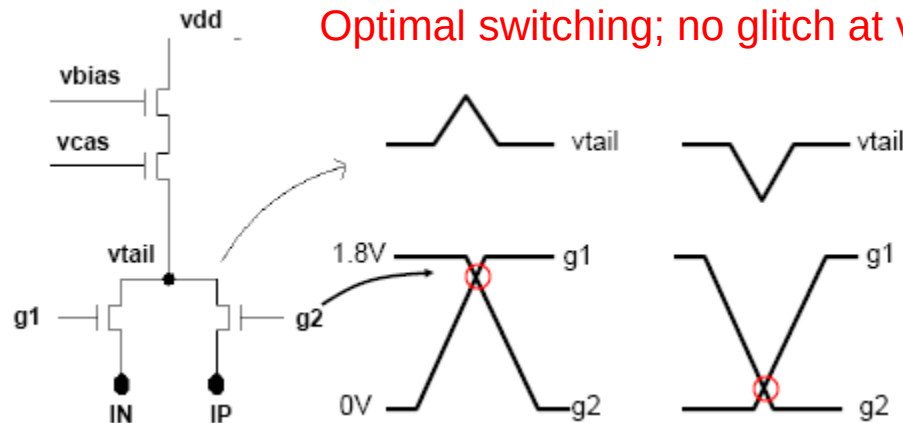

Gate Drive Crossover Control Loop

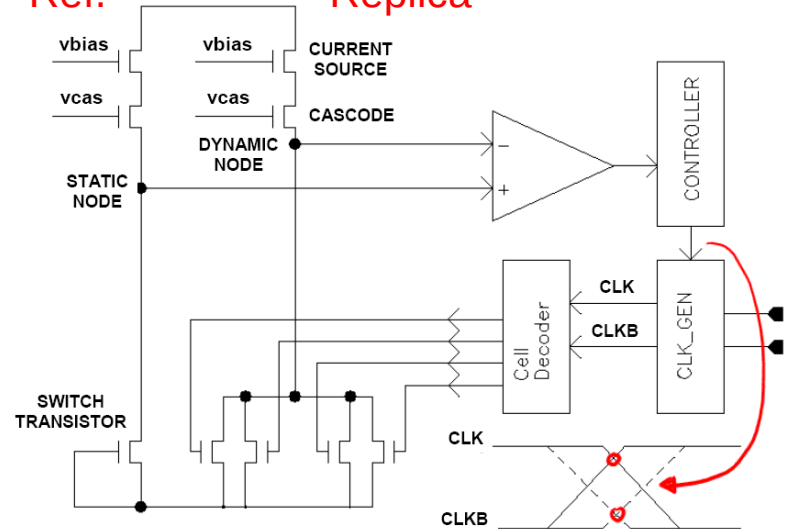


[Schaffner, ISSCC 2004]

Measurements

Max Sample Frequency	1.4	GSPS
Resolution	14	Bit
DNL	+/- 0.8	LSB
INL	+/- 2.1	LSB
SFDR @ 1.0 GSPS	> 60	dB
IMD @ 1.0 GSPS	> 64	dBc
NSD @ $f_{out} = 400\text{MHz}$	-155	dBm/Hz
Power (Core) @ 1.4GSPS	200	mW
Power(Total) @ 1.4GSPS	400	mW
Area (Core)	0.8	mm ²
Area (Chip)	6.25	mm ²



2 Tone Intermodulation Distortion

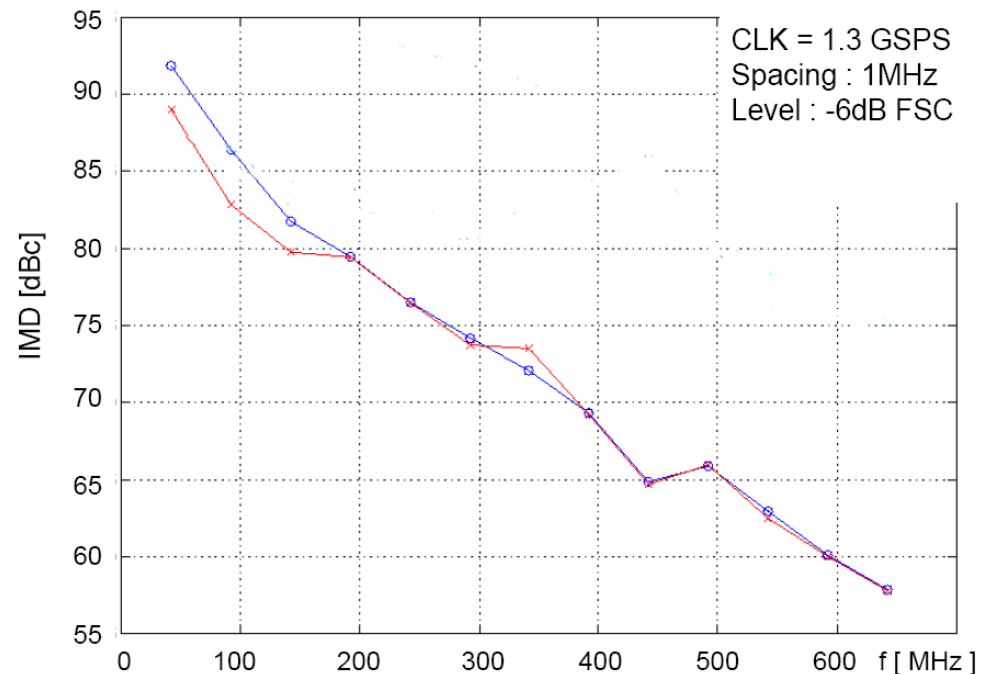


[Schafferer, ISSCC 2004]

High Performance DAC Example #4



Technology	65nm CMOS
Number of Bits	12
Conversion speed	2.9 GS/s
INL	0.5 lsb
DNL	0.3 lsb
R_{load}	50 Ω
$I_{tail,total}$	50 mA
Voltage Swing	2.5 V _{ppd}
Power Dissipation	188 mW
Area	0.31 mm ²

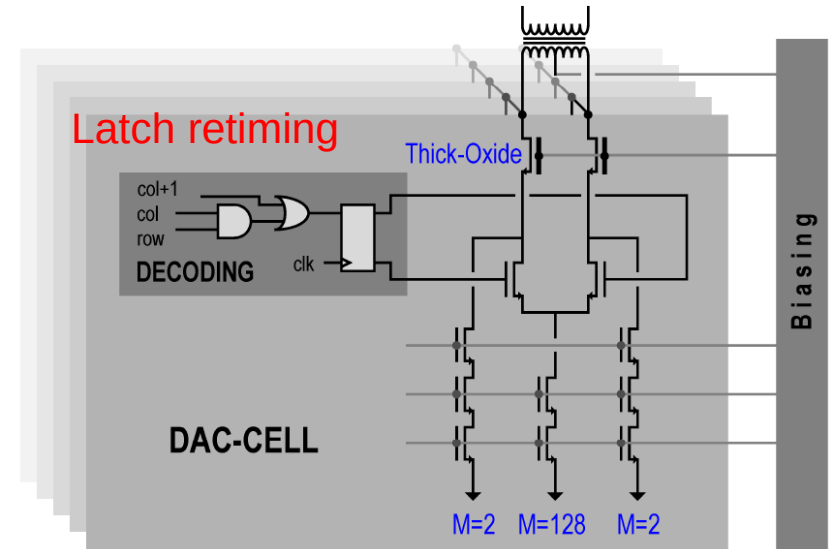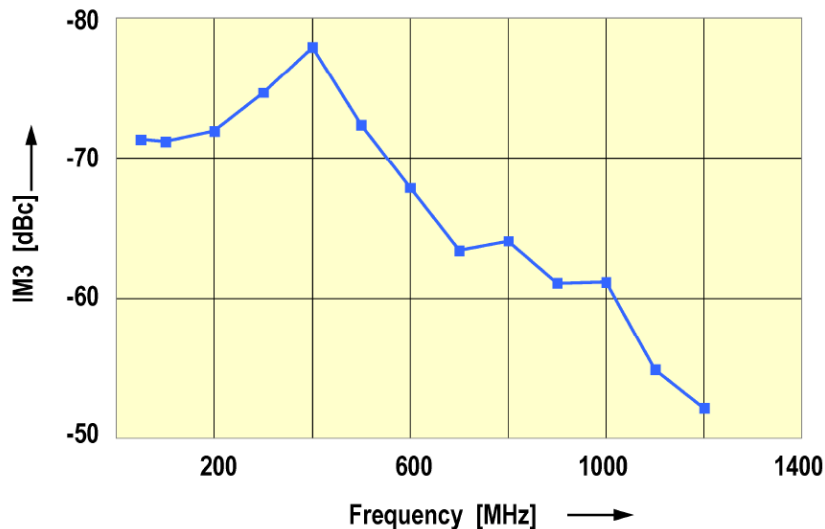

[Lin, ISSCC 2009]

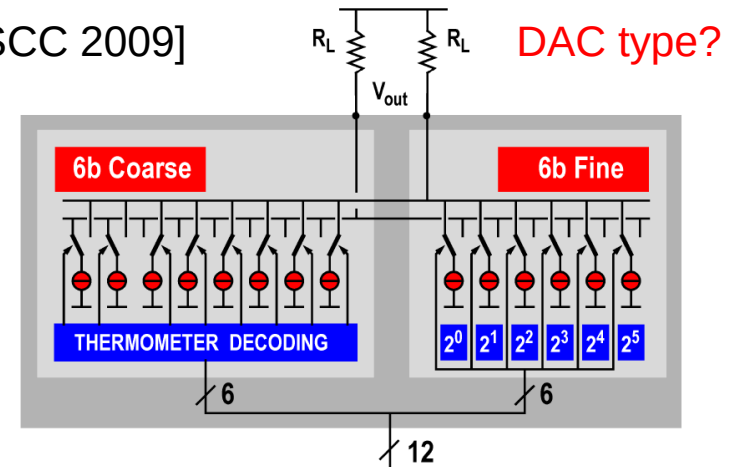

High Performance DAC Example #5

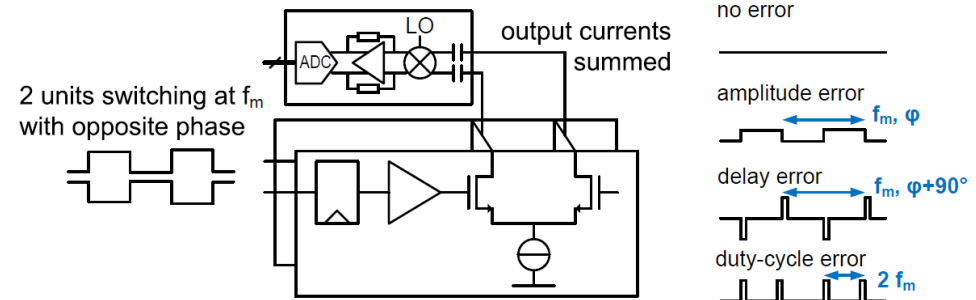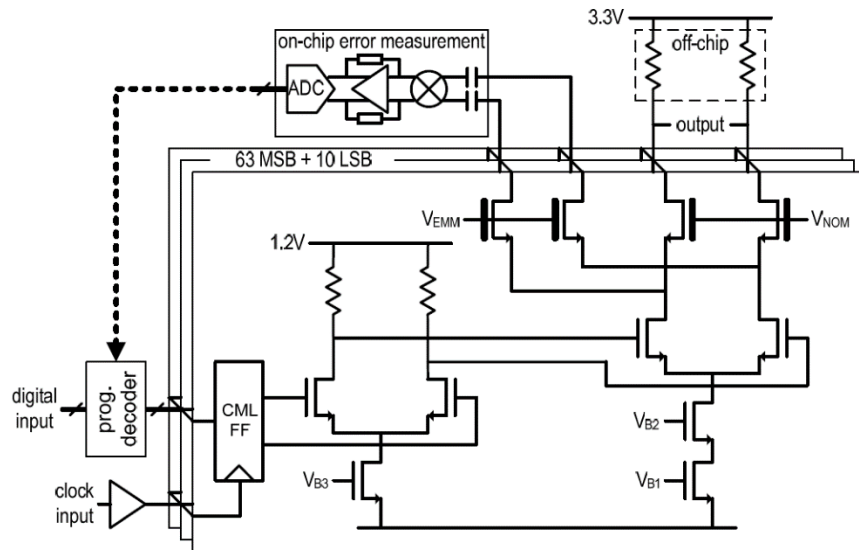

Error signal down-converted to DC, filtered and digitized


- $f_{LO} = f_m$ & $\phi_{LO} = \phi \Rightarrow$ amplitude error
- $f_{LO} = f_m$ & $\phi_{LO} = \phi + 90^\circ \Rightarrow$ delay error
- $f_{LO} = 2 f_m \Rightarrow$ duty-cycle error

[van de Vel, ISSCC 2014]


[Tang, JSSC11]

Sort and combine



Example: 3b DAC

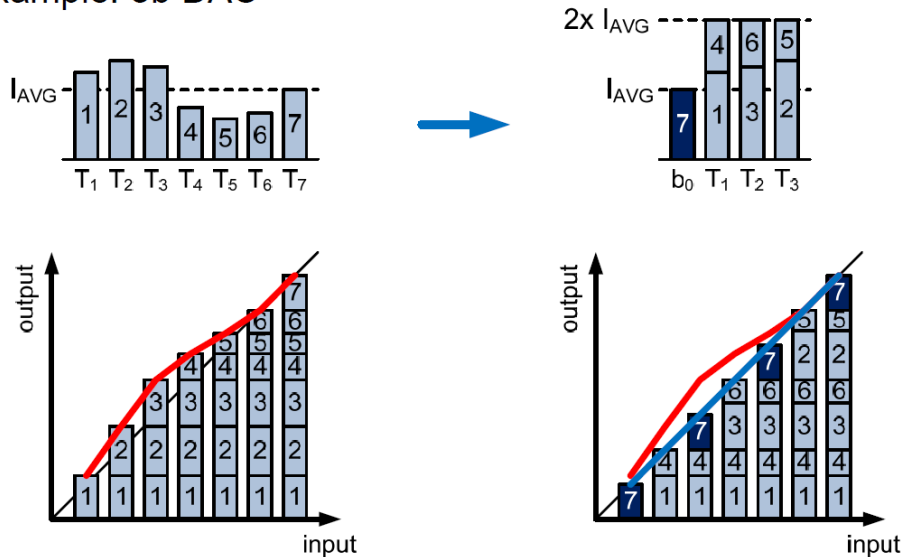

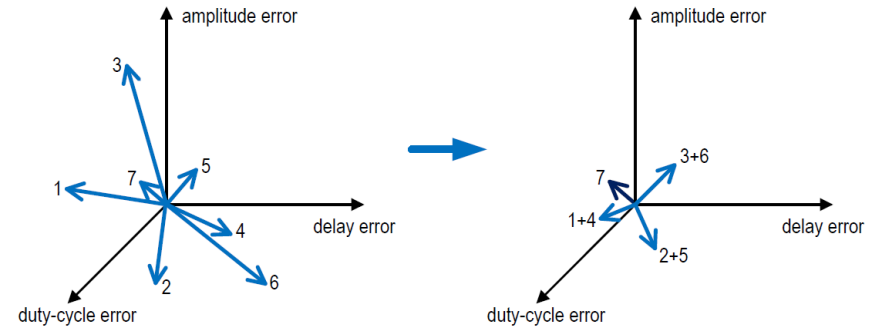3D unit matching errors represented as 3D error vectors:




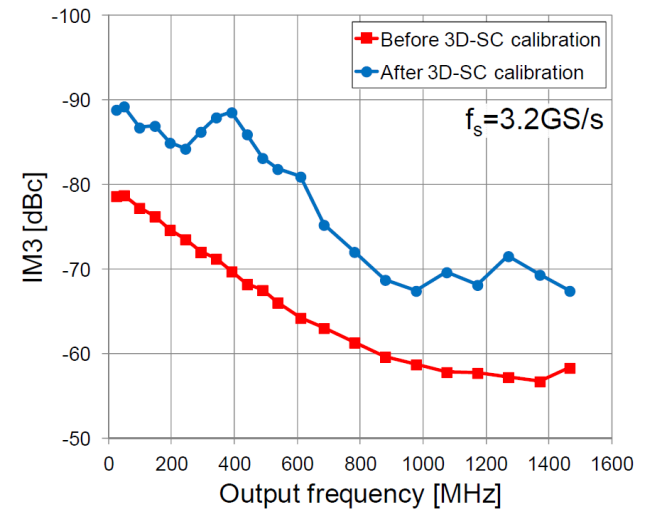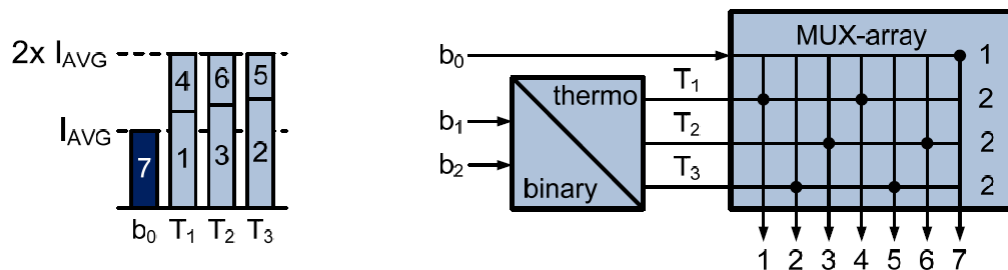Sort-and-combine to combinations of 2 units:



[van de Vel, ISSCC 2014]

High Performance DAC Example #6

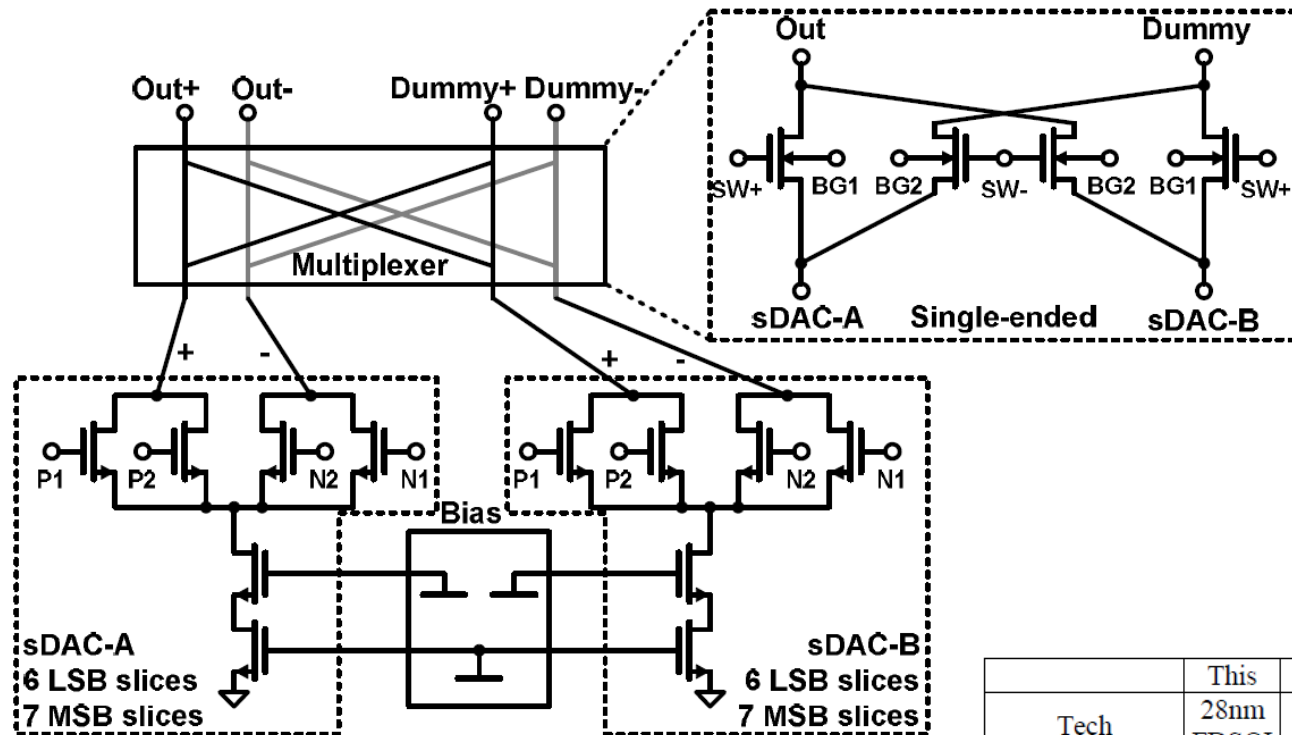

[Nauta, VLSI 2014]

	This	[1]	[2]	[3]	[4]	[5]
Tech	28nm FDSOI	28nm	180nm	65nm	65nm	65nm
Resolution [Bits]	9	13	14	12	9	6
Power [mW]	110	375	>600	70	60	750
V_{supply} [V]	1.0	1.8	-1.5/1.8	1.2	1.2	1.1/2.5
Area [mm ²]	0.04	1.16	4	0.4	0.04	0.24
Swing [$V_{\text{pp-diff}}$]	0.425	N/A ^b	1.0	0.5	0.4	0.6
F_s [GHz]	11	9	6	1.7	3	56
SFDR ^a [dB]	51	-	52	58	49	43
IM3 ^a [dBc]	-51	-44	-65	-62.5	-60	-